



Reg. No. :

Name :

Combined First and Second Semester B.Tech. Degree
Examination, April 2014
(2013 Scheme)

13.108 : BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (FR)


Time : 3 Hours

Max. Marks : 100

PART – A

Answer all questions.

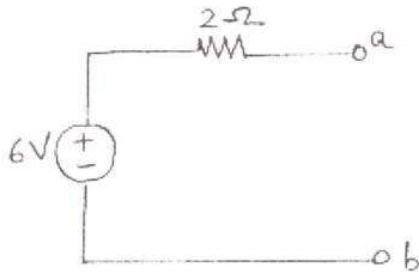1. Explain Kirchoff's law.
2. Convert the given voltage source circuit to current source circuit.



3. State and explain Reciprocity theorem.
4. Define the bandwidth of a series resonant circuit.
5. If the current through a coil having an inductance of 0.5H is reduced from 5A to 2A in 0.05s, calculate the mean value of emf induced in the coil.
6. Three resistor 10Ω , 20Ω and 25Ω are connected in star. Find their equivalent delta circuit.
7. Plot the VI characteristics of a zener diode.
8. Obtain the relationship between α and β of a transistor.
9. Explain briefly about the losses in a transformer.
10. Draw the block diagram of SMPS.

(2×10=20 Marks)

P.T.O.




PART - B


Answer **one full** question from **each** Module.

Module - I

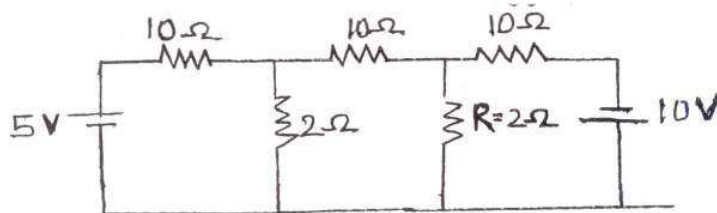
11. a) Find the voltage across resistor R, in the network by mesh analysis. 10



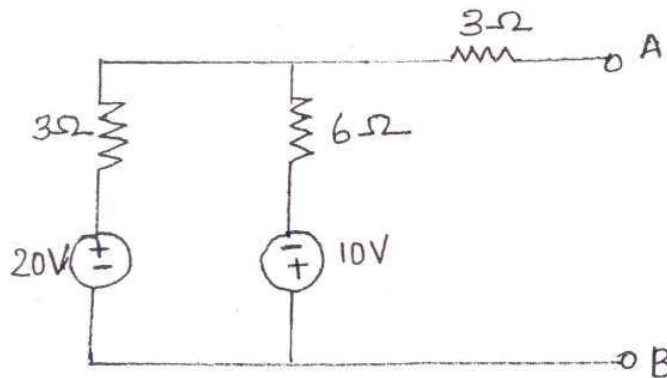- b) Obtain the thevenin and Norton equivalent circuit for the active network given below in figure 10



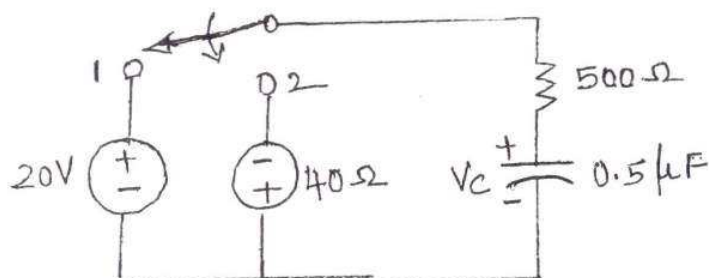12. a) The switch in the circuit is closed one position 1 at $t = 0$ and moved to position 2 after 1 time constant, at $t = \tau = 250 \mu\text{s}$. Find the expression for current at $t > 0$ and plot the current wave form. 10





b) A series RLC circuit has $R = 2\Omega$ and $C = 200\mu F$. Applied voltage = 10 v at a frequency of 1000 rad/sec. The inductance is varied so that circuit is in resonance.

Find the value of

- 1) inductance at resonance
- 2) quality factor and
- 3) bandwidth.

10

Module – II

13. a) Explain the following terms with respect to magnetic circuit.

- 1) mmf
- 2) flux density
- 3) field strength
- 4) reluctance.

10

b) A circular iron ring of mean diameter 25 cm and cross sectional area 9 cm^2 is wound with a coil of 100 turns and carries a current of 1.5 A. The relative permeability of iron is 200. Calculate the amount of flux produced in the ring.

6

c) Express the admittance of the circuit having the following impedances in rectangular notation

- a) $(3 + j5)\Omega$
- b) $20\angle -30^\circ$

4

14. a) Explain the following terms w.r.t. a waveform

- 1) RMS value
- 2) Average value
- 3) Form factor.

8

b) Draw the block diagram of a CRO.

5

c) Explain the working principle of a moving coil ammeter.

7

**Module – III**

15. a) Derive the emf equation of a transformer. 5
- b) A 125 kVA transformer having primary voltage of 2000 V at 50 Hz has 182 primary and 40 secondary turns. Neglecting losses calculate
- 1) full load primary and secondary current
 - 2) no load secondary emf. 5
- c) Explain the working of a single phase induction motor. What are the different methods for starting single phase induction motor ? Explain any one method. 10
16. a) Explain the necessity of earthing. Explain any one method of earthing with the help of a neat diagram. 10
- b) Explain the working of ELCB with the help of a neat circuit. 10

Module – IV

17. a) With the help of a neat diagram explain the working of a half wave rectifier. Also plot the input and output waveform. 10
- b) Compare the three different configuration of bipolar junction transistor. 10
18. a) Explain the following :
- a) SCR
 - b) Photodiode
 - c) Solar cell
 - d) LED 10
- b) Explain the construction and working of an n-channel. JFET using a neat diagram. 10
-