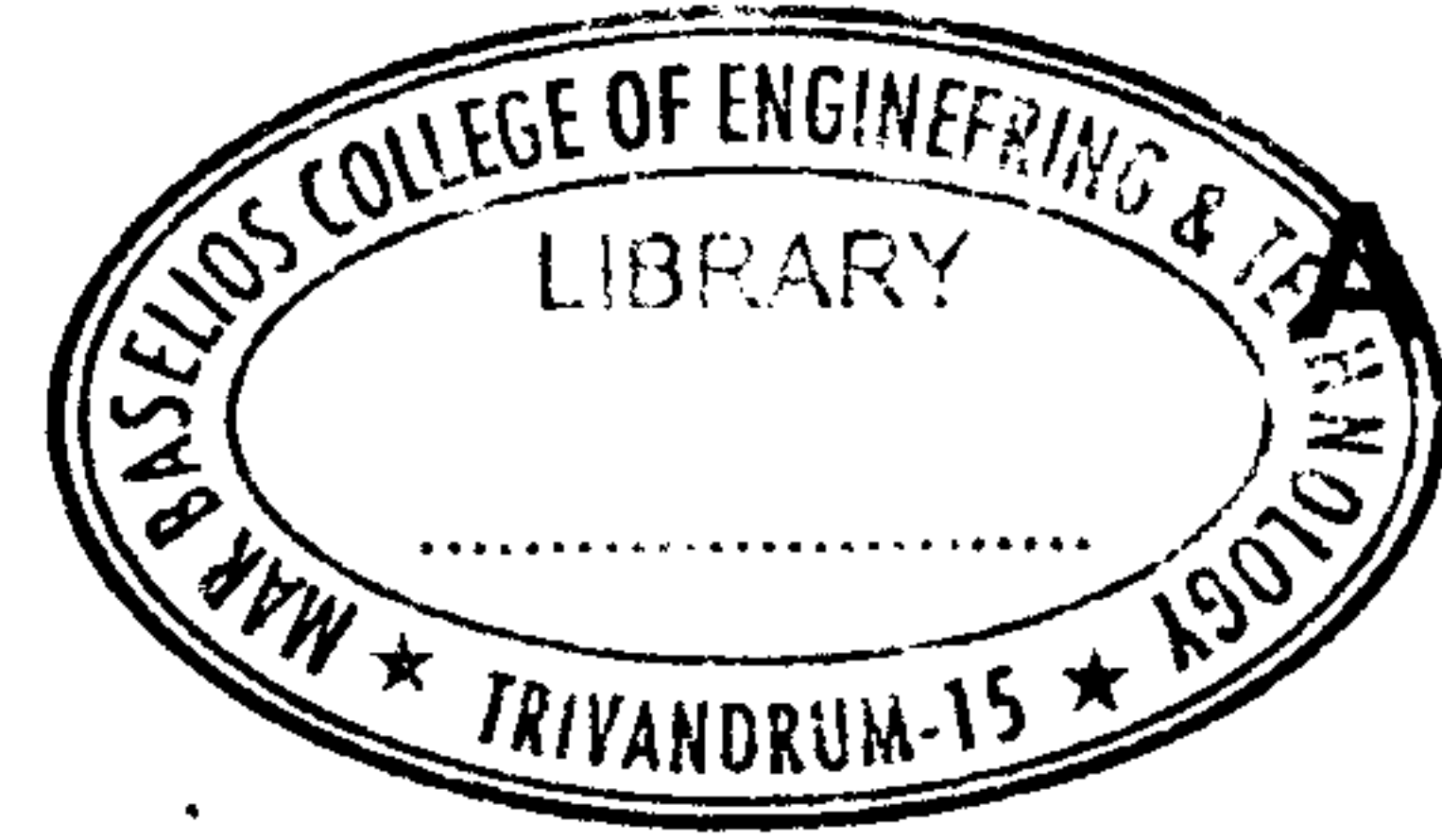




(Pages : 4)



6344

Reg. No. :

Name :

**Third Semester B.Tech. Degree Examination, September 2016
(2008 Scheme)**

08.303 : NETWORK ANALYSIS (TA)


Time : 3 Hours

Max. Marks : 100

PART - A


Answer **all** questions :

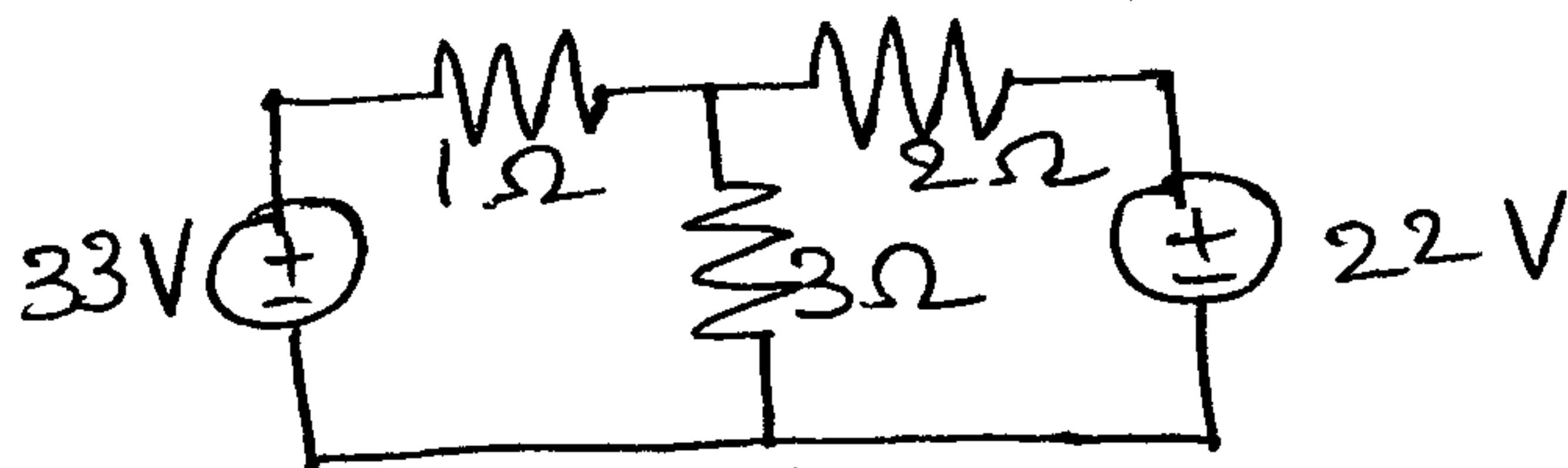1. Find the current flowing through 3Ω resistor in the network using Millman's theorem.



2. Plot the following functions :

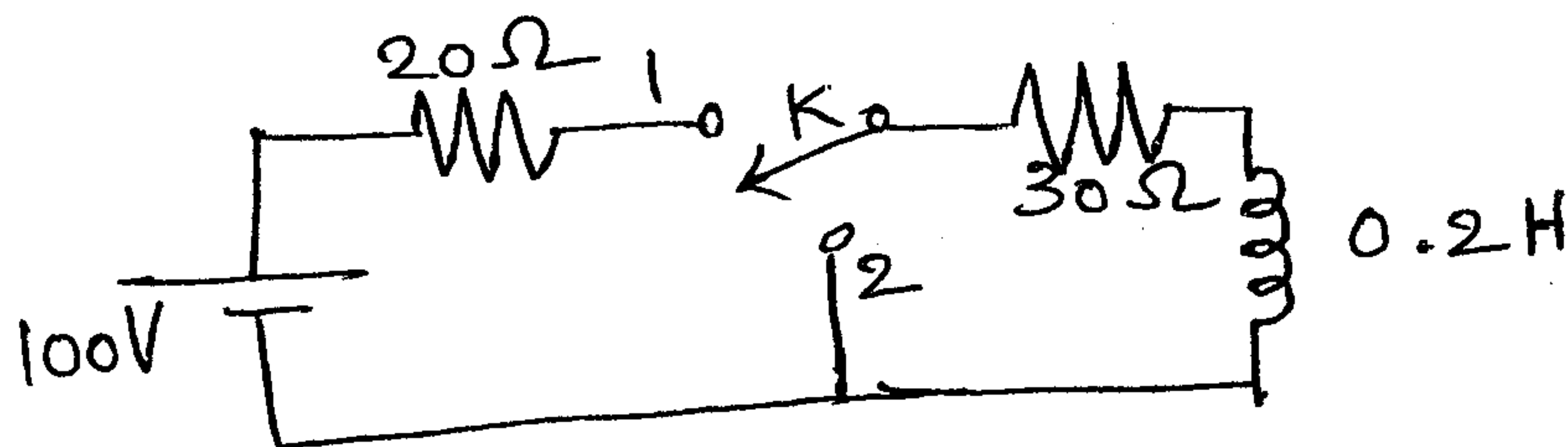
- i) $u(t - 5) + u(t - 2)$
 - ii) $2u(t) - u(t - 3)$
 - iii) $4r(t - 2)$
 - iv) $s(t - 4)$
3. Verify the initial value and final value theorem for $f(t) = 5e^{-3t} \cos 5t$.
4. For the circuit shown, find the current equation for $t > 0$, when the switch k is moved from position 1 to 2 at $t = 0$. Assume that the circuit is in steady state before $t = 0$.



P.T.O.



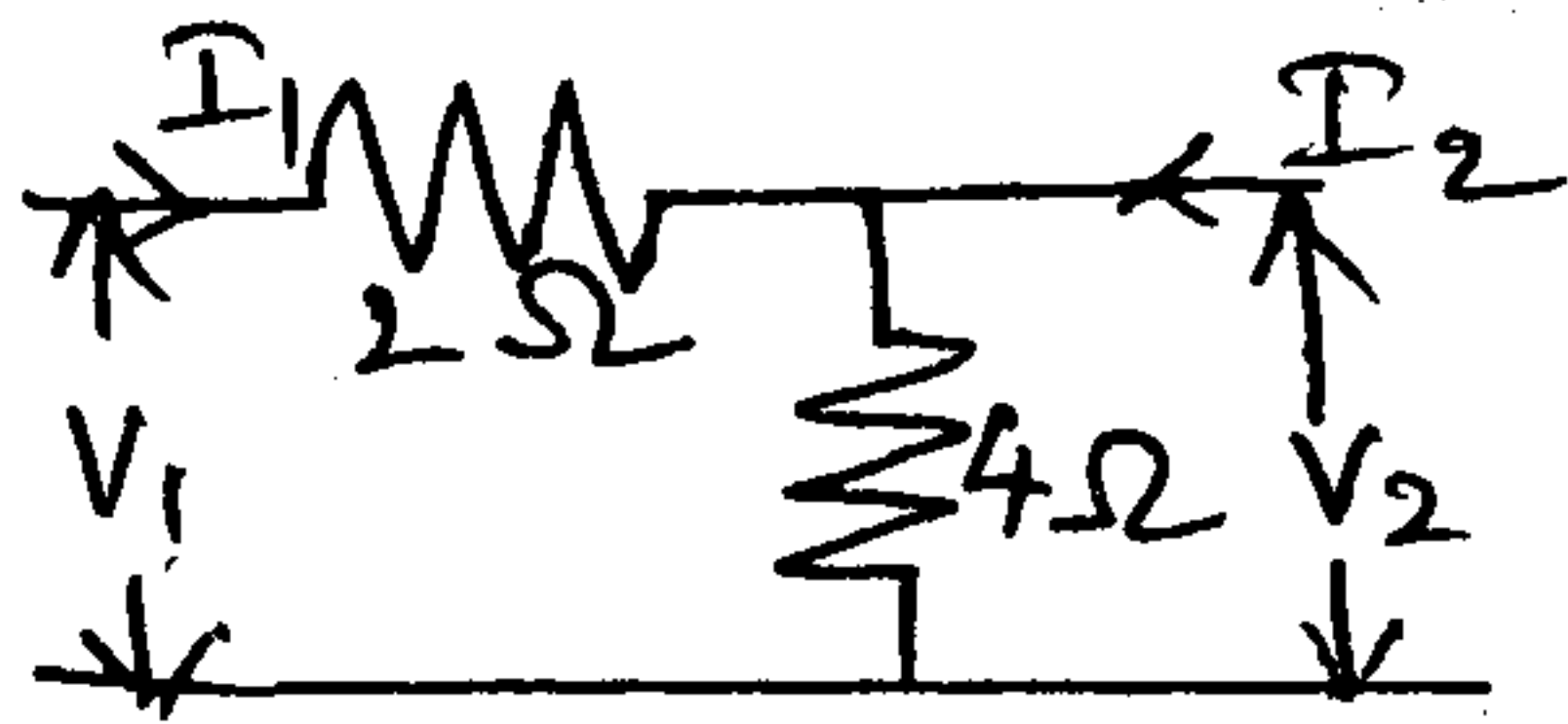5. Find the transmission parameters of the network



6. Distinguish between image impedance and characteristic impedance.
7. Obtain the Nyquist plot of the transfer function, $G(j\omega) = \frac{1}{1+j\omega T}$ is a semicircle when the frequency, ω is varied from 0 to infinity.
8. A series RLC circuit consists of $R = 50\Omega$, $L = 0.2H$ and $C = 10\mu F$ and an applied voltage of 20V. Determine the resonant frequency, Q-factor and bandwidth of the circuit.
9. Show that in a series RLC circuit, $f_0 = f_L \cdot f_H$, where f_L , f_H are half-power frequencies and f_0 is the resonant frequency.
10. Explain the significance of frequency transformation in analog filter design.


(10×4=40 Marks)

PART - B

Answer **any two** questions from **each** Module. **Each** question carries **10** marks :


Module - I

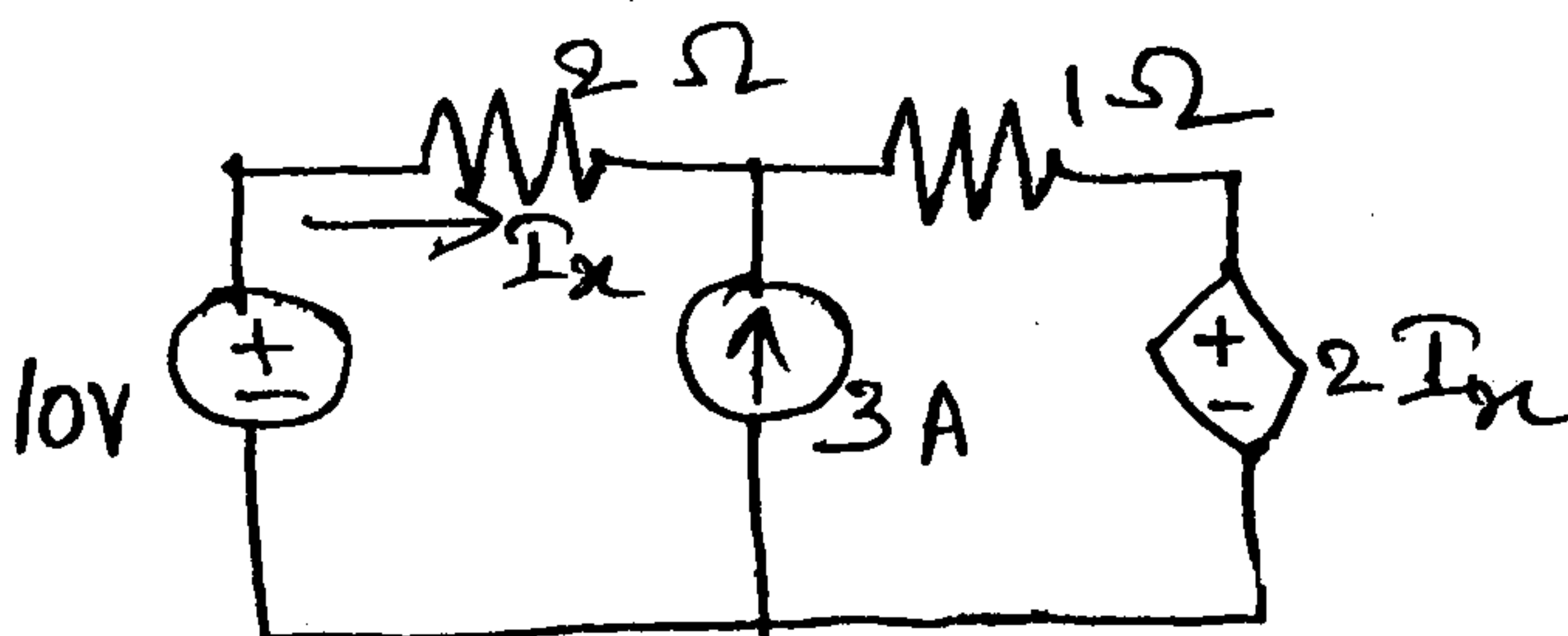11. Find the current I_x using Thevenin's theorem.







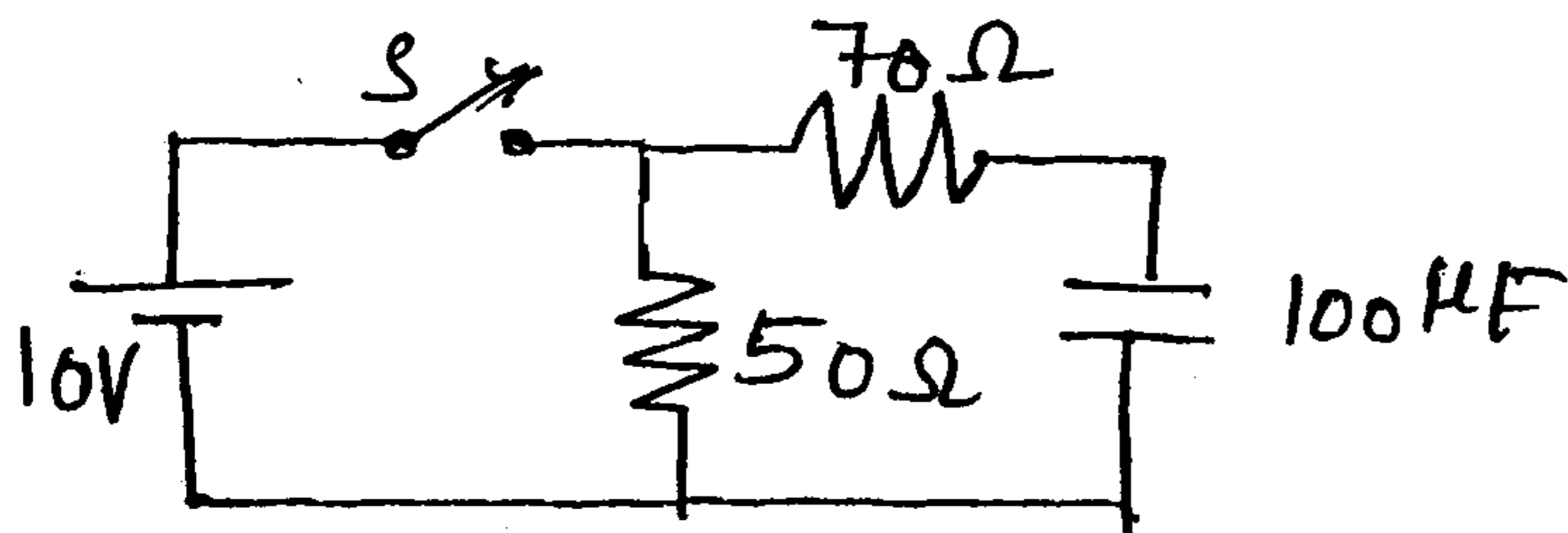12. In the circuit shown, the switch S is closed at $t = 0$. Find the time when the current from the battery reaches 500 mA.




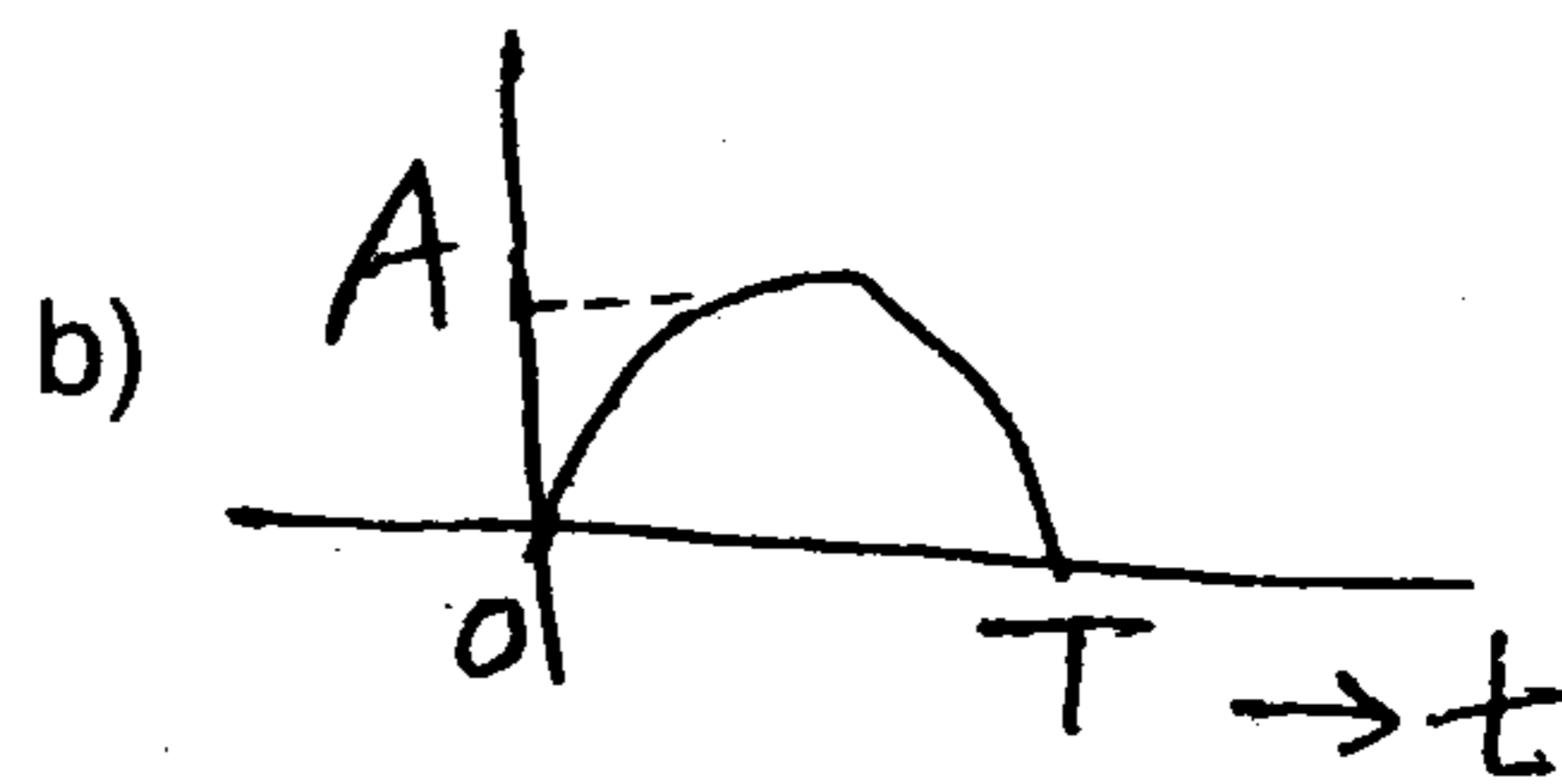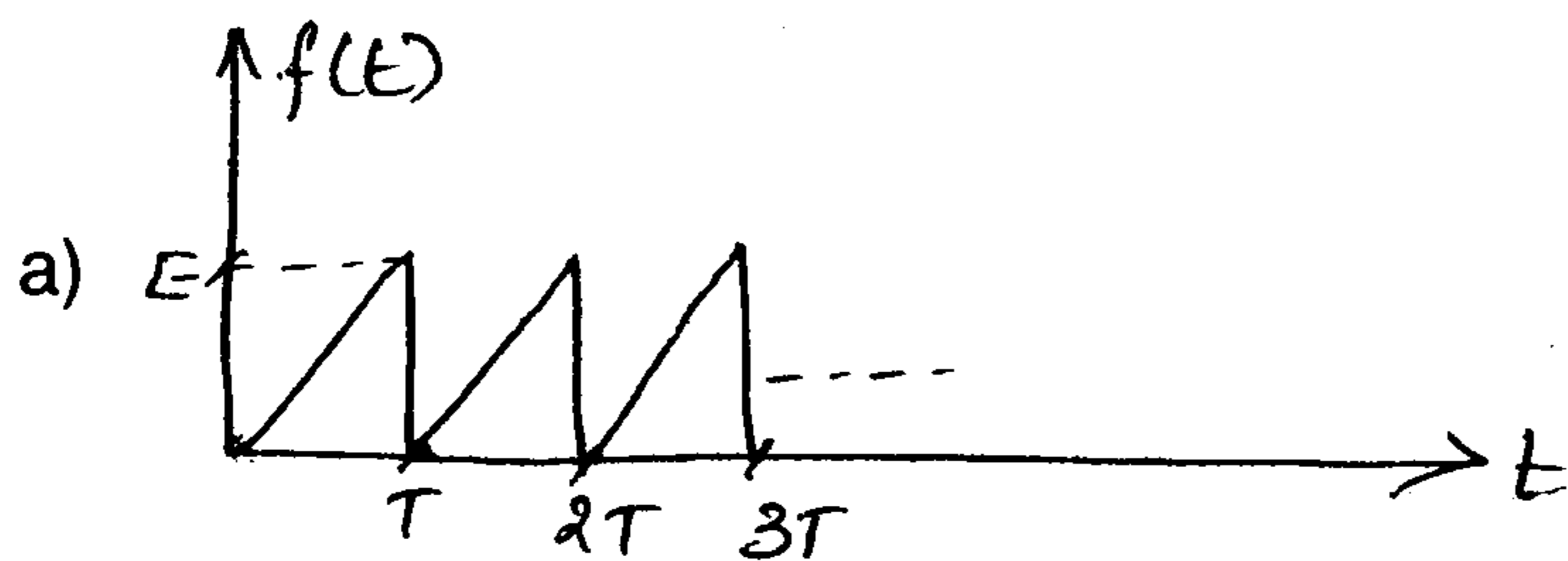13. Find the Laplace transform of the given waveforms.



Module - II

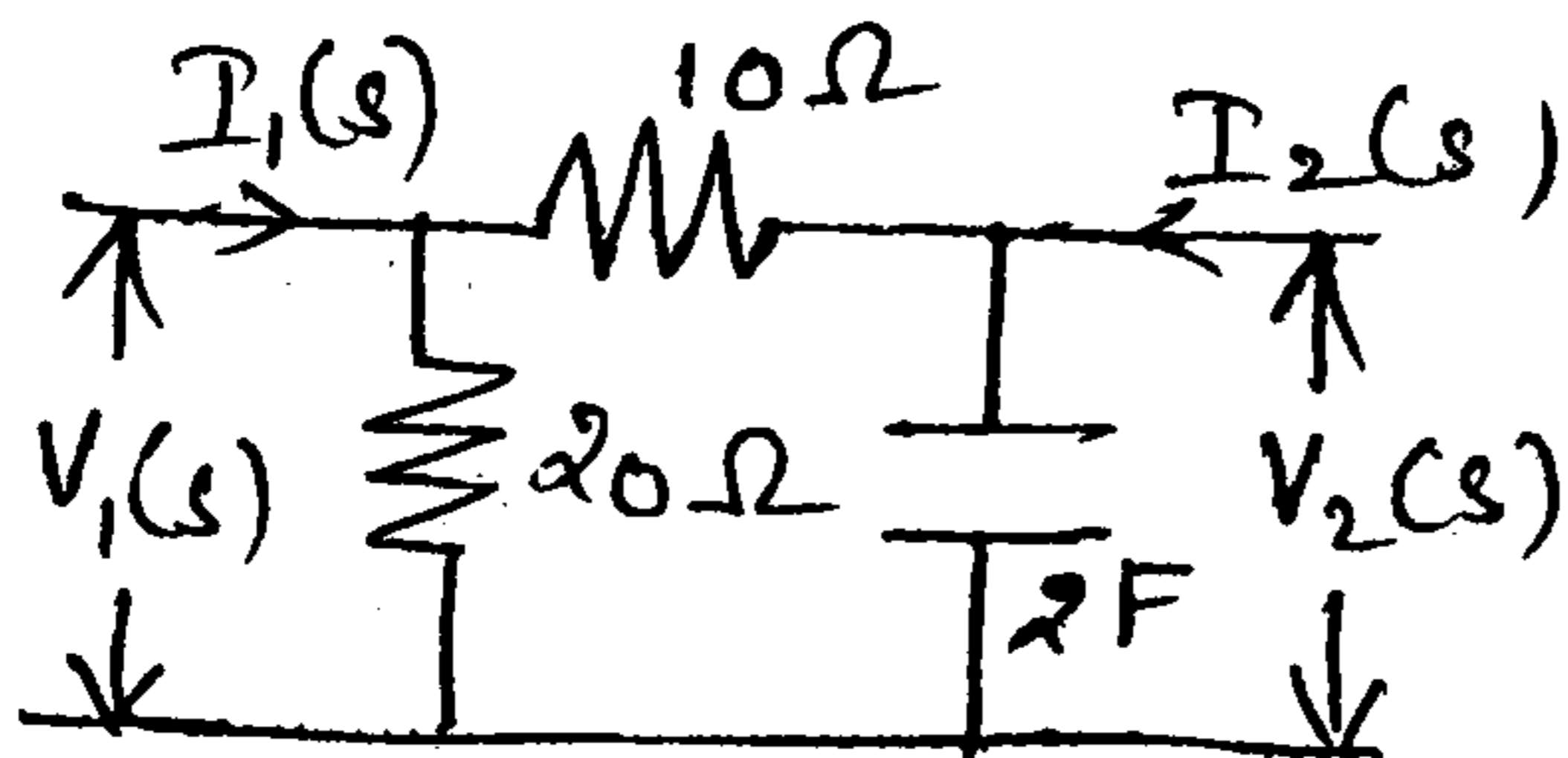14. For the network shown, find the driving point impedance, $Z_{11}(s)$, transfer impedance, $Z_{21}(s)$ and voltage transfer ratio, $G_{21}(s)$.




15. Draw the Bode plot for the transfer function, $G(s) = \frac{4}{s(1 + 0.5s)(1 + 0.08s)}$, From

the Bode plot, determine

- 1) Phase-cross over frequency
- 2) Gain cross over frequency
- 3) Gain margin
- 4) Phase margin.




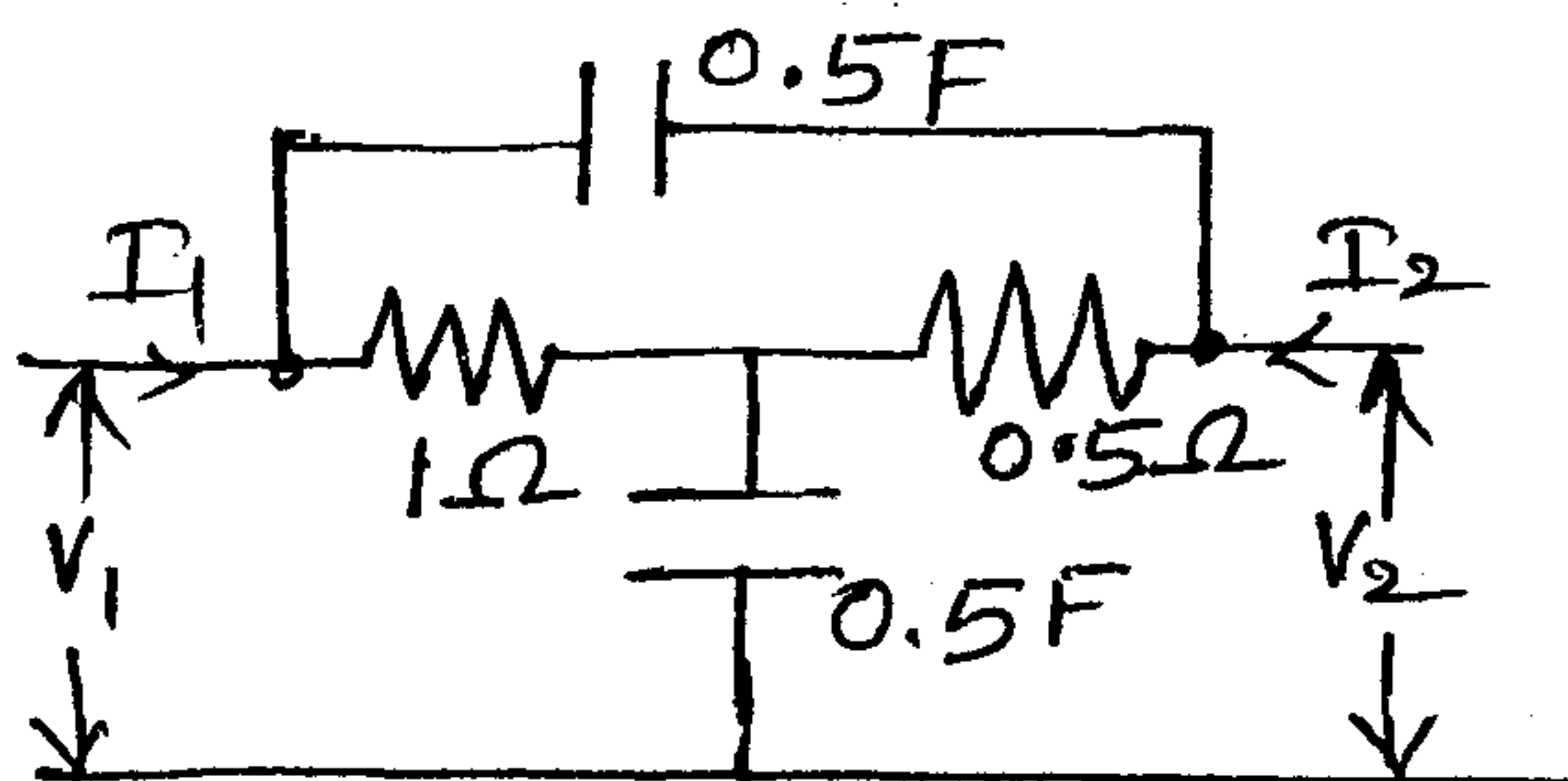16. Determine the admittance parameters of the network.




Module - III

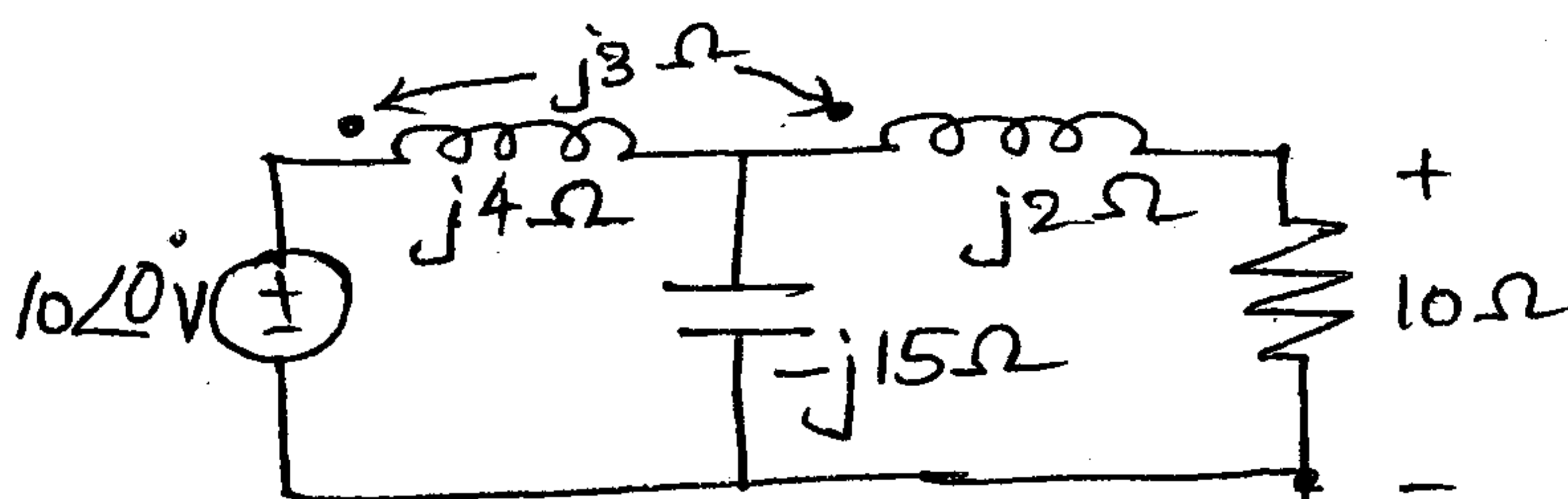17. Find the voltage across the 10Ω resistor of the coupled circuit shown below :



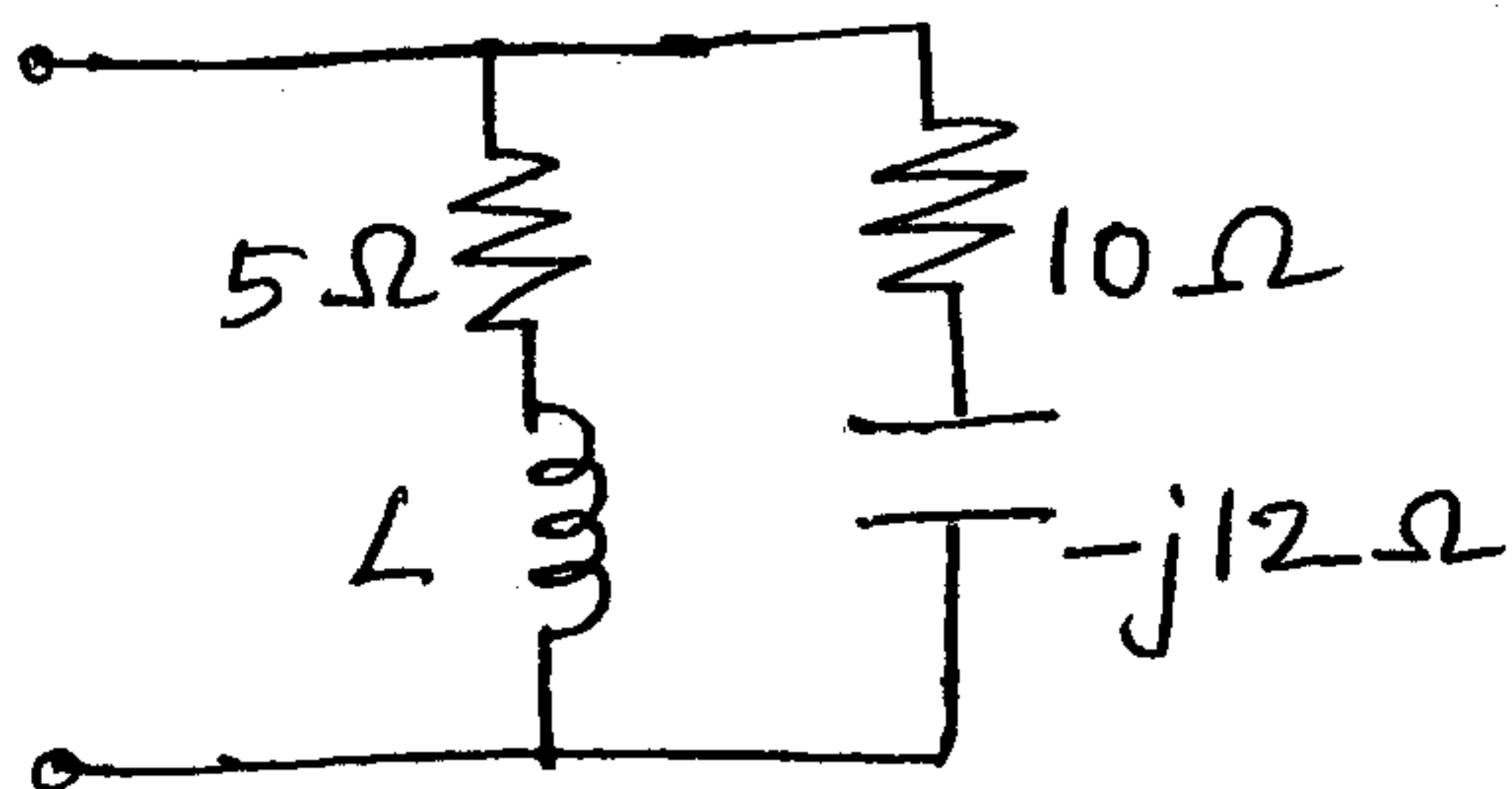18. Find the value of L at which the circuit resonates at a frequency of 1000 rad/sec .



19. Find the order and cut-off frequency of a Butterworth to meet the following specifications.

Pass band gain = - 1dB

Pass band = 0 to 1.75 MHz

Stop band loss = at least 20 dB at 2.5 MHz.

(6×10=60 Marks)

