

Reg. No. :

Name :

**Third Semester B.Tech. Degree Examination, April 2015
(2013 Scheme)**

13.305 : ELECTRONIC CIRCUITS (T)


Time: 3 Hours

Max. Marks: 100

PART – A

Answer **all** questions. **Each** question carries **2** marks.

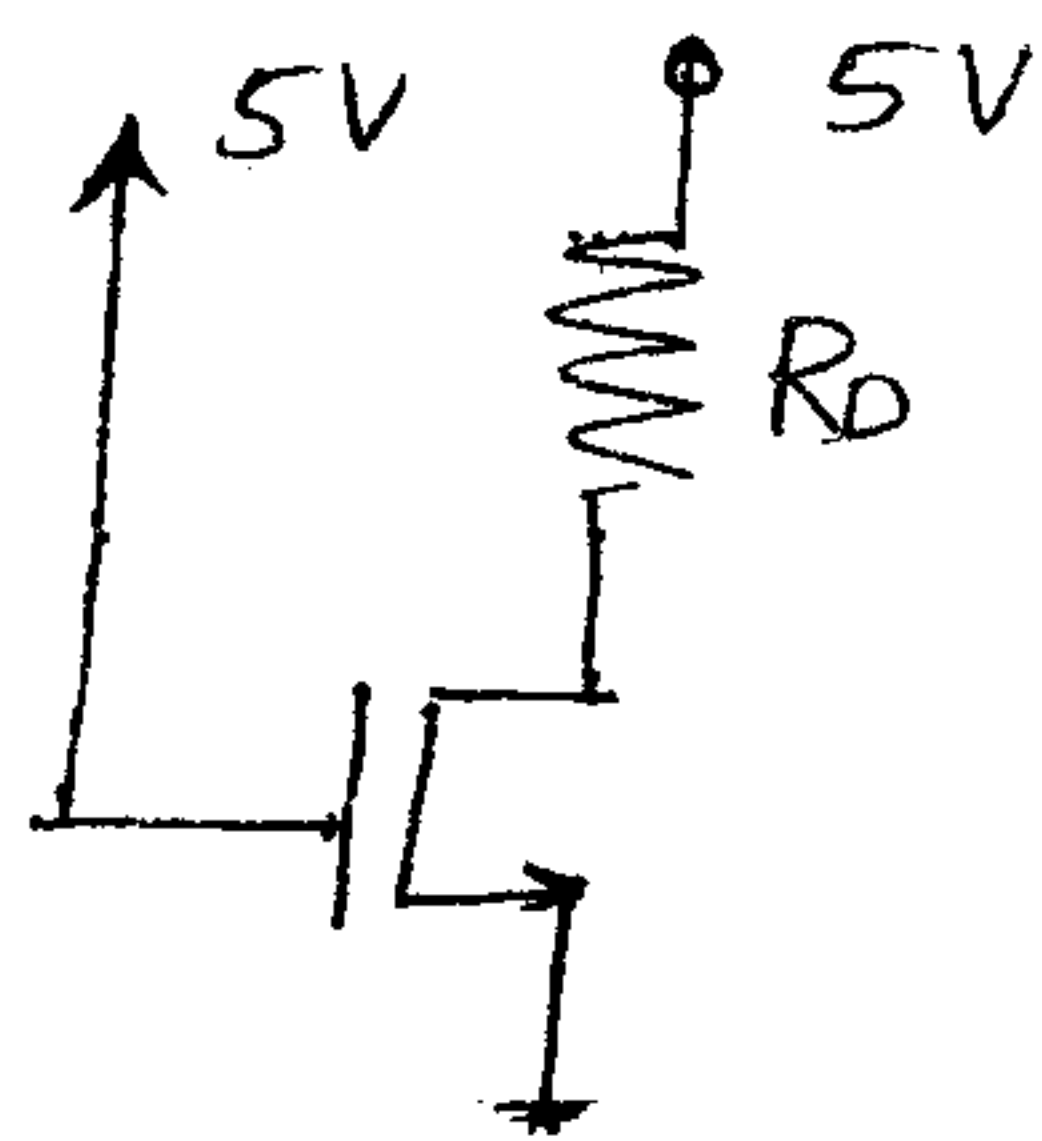1. Explain how a LPF acts as an integrator.
2. Obtain the circuit of a double clipper clipping at +3 and – 3 volts. Assume ideal diodes.
3. Calculate the bandwidth and capacitance C_{π} of a bipolar transistor. $f_T = 500$ MHz at $I_C = 1$ mA, $\beta_0 = 100$ $C_y = 0.3$ PF.
4. Draw the small signal equivalent of MOSFET including body effect.
5. Explain why voltage divider biasing is preferred over other biasing circuits.
6. Design the circuit to establish a drain voltage of 0.1V, $V_t = 1$ V, $K_n = 1$ mA/V².



7. Compare the different feedback topologies.
8. Differentiate between synchronous tuning and stagger tuning.
9. Write down expressions for ripple factor of a bridge rectifier and full wave rectifier.
10. Draw a current mirror circuit. **(10×2=20 Marks)**




PART - B

Answer any one question from each Module. Each full question carries 20 marks.

Module - I



11. a) Calculate A_v , R_i and R_o of the circuit. Given $\beta = 100$, $V_{BE} = 0.7 \text{ v}$ and $V_A = 80 \text{ V}$.

10

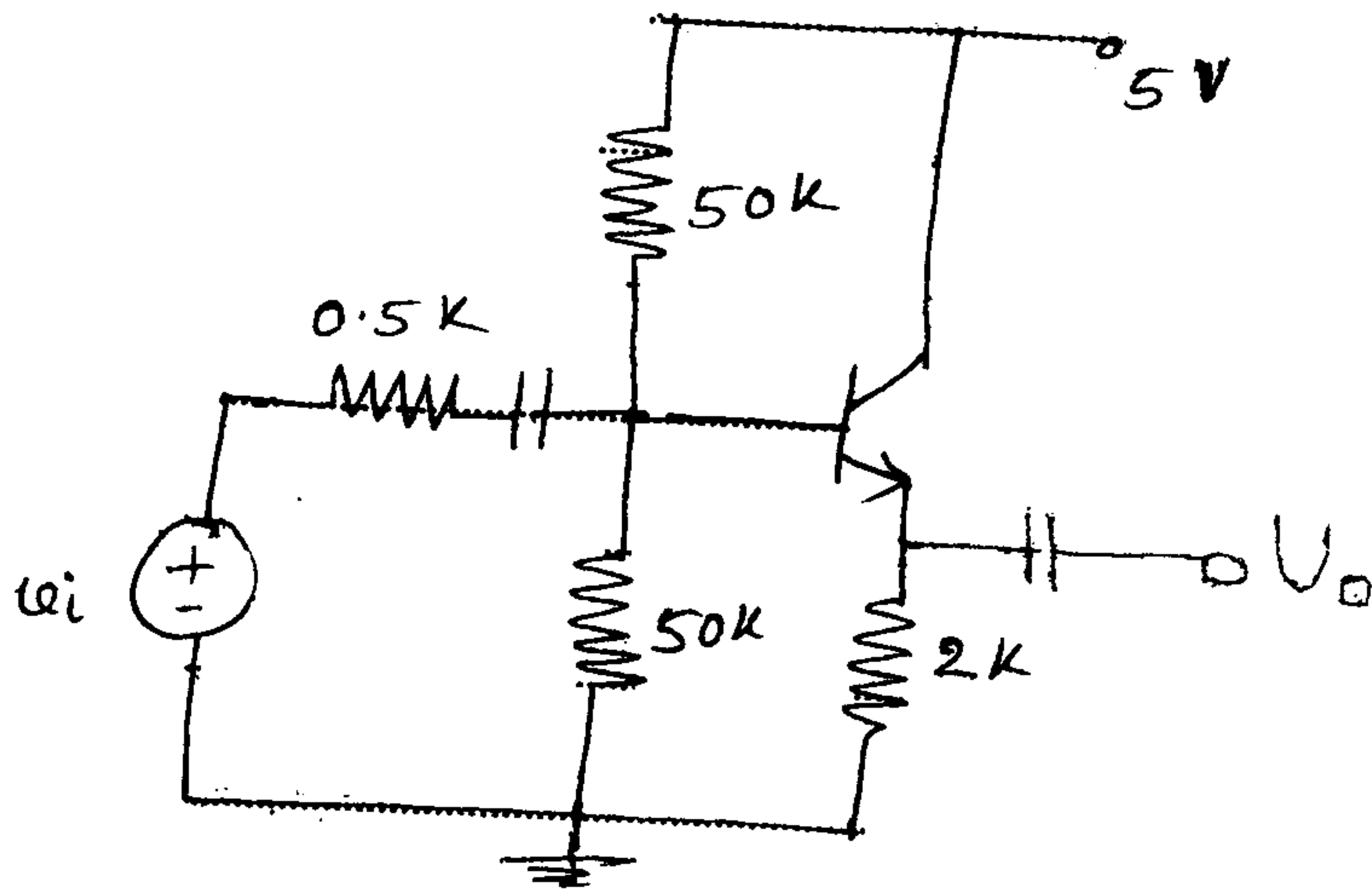


- b) Determine voltages at all nodes and current through all branches of the following circuits.

(4+6=10)

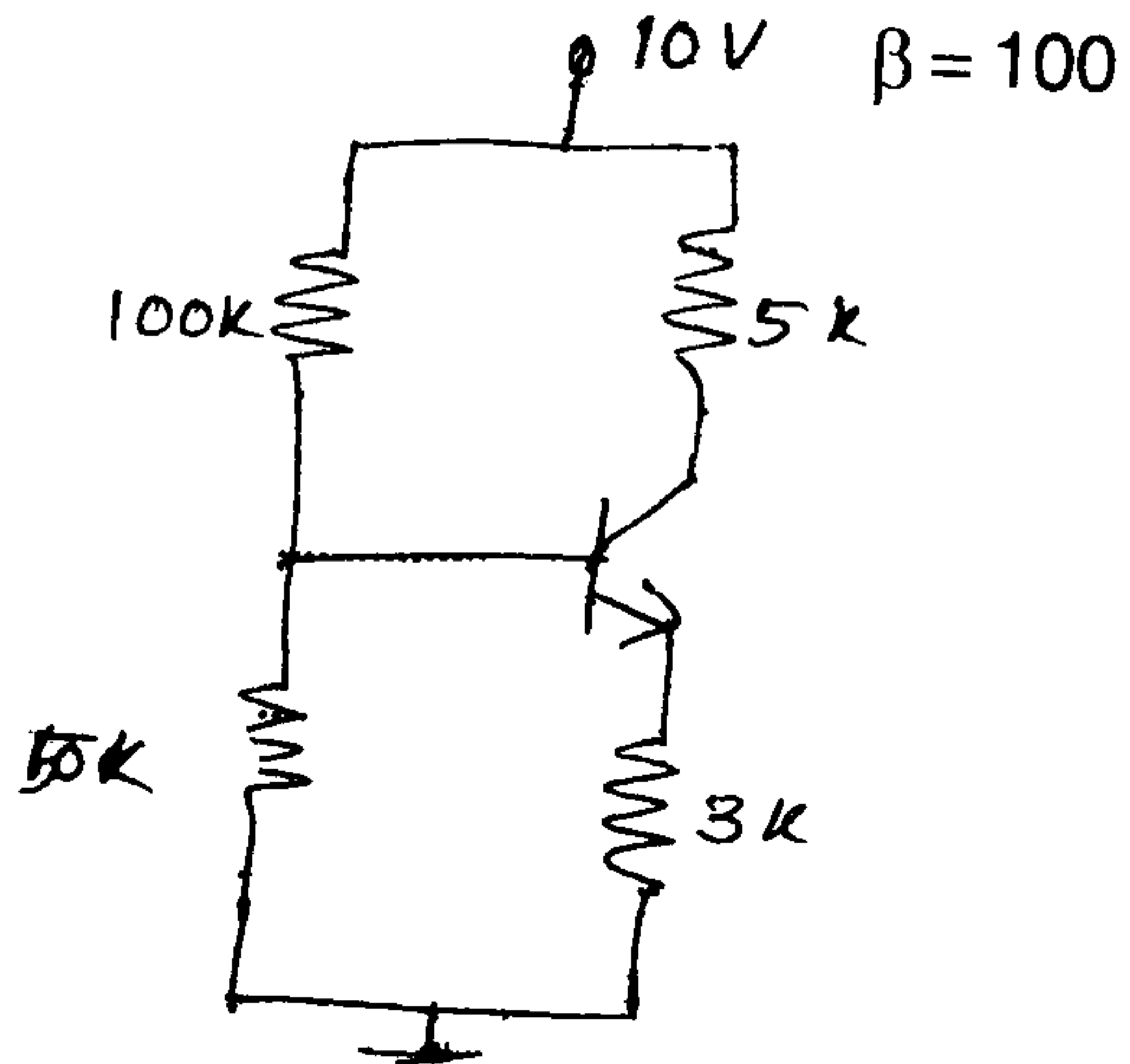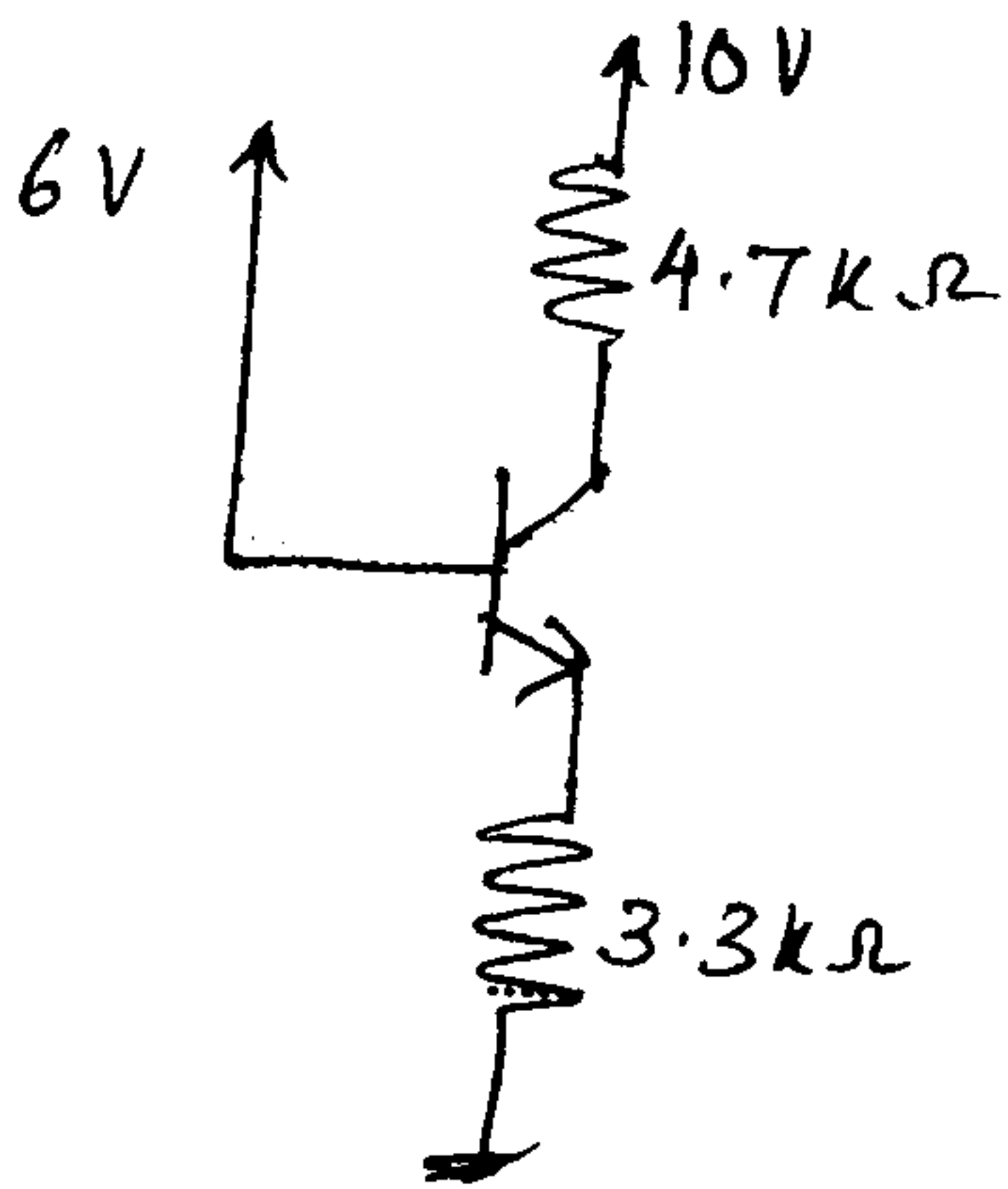



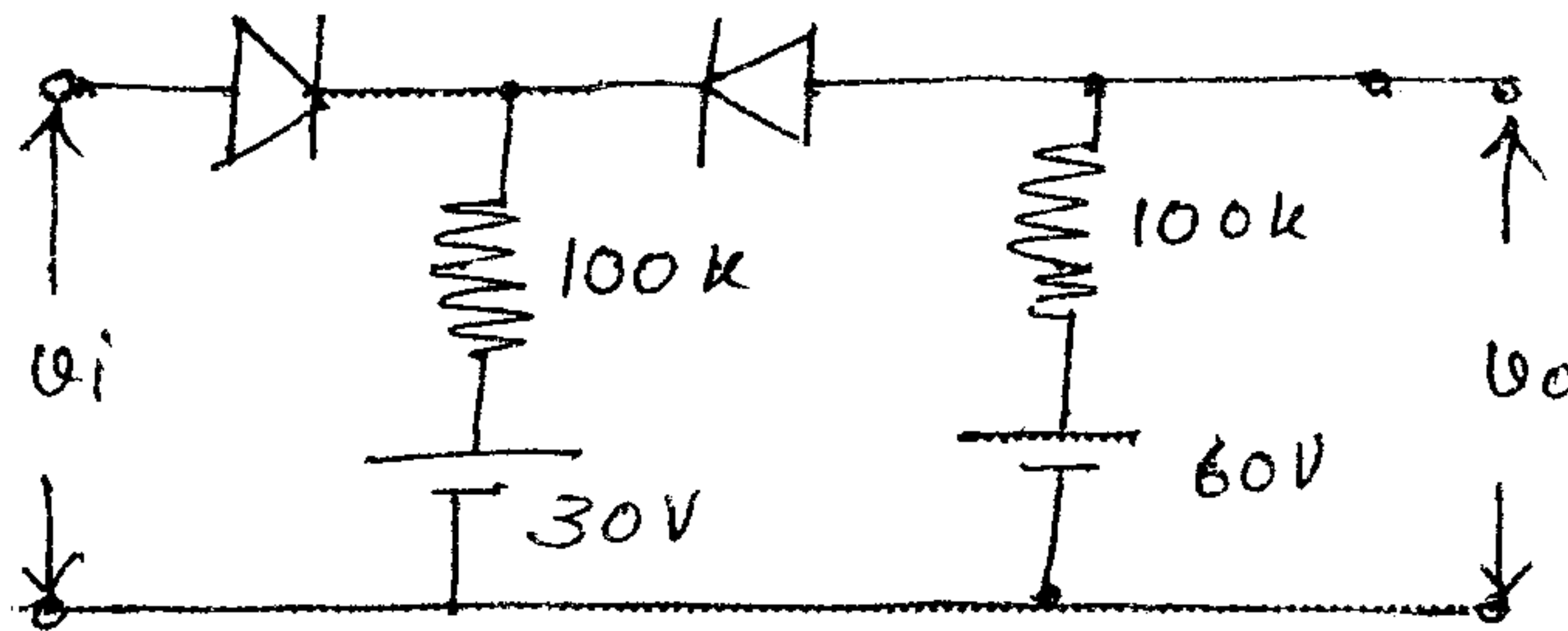12. a) Draw the transfer characteristics of the clipping circuit shown. The input varies linearly from 0 to 125 V. Plot the output. 10




- b) With neat circuit diagram explain an RC coupled amplifier, functions of different components and its frequency response. 10

Module – II

13. a) For the circuit shown the NMOS transistor parameters are $V_t = 1V$, $K_n = 3 \text{ mA/V}^2$ and $\lambda = 0$. Determine: 12

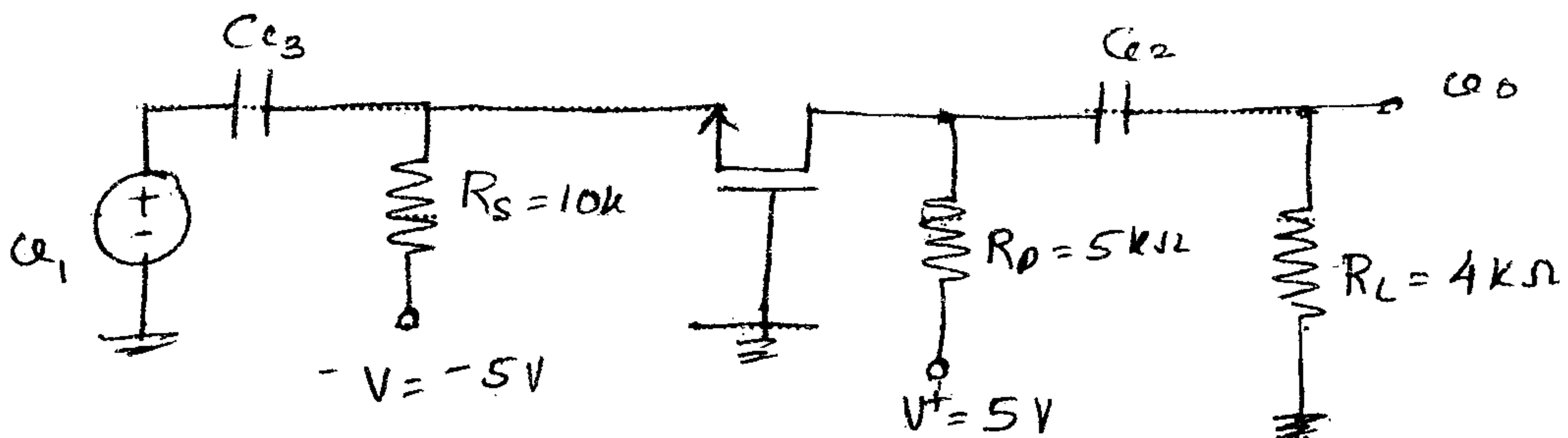- a) I_{DQ} and V_{DQ} and
b) Find the small signal voltage gain.




- b) Explain current source biasing of MOSFET. Discuss on current mirror circuit. 8

14. a) Obtain expression for voltage gain, input impedance and output impedance of a CD amplifier. 10





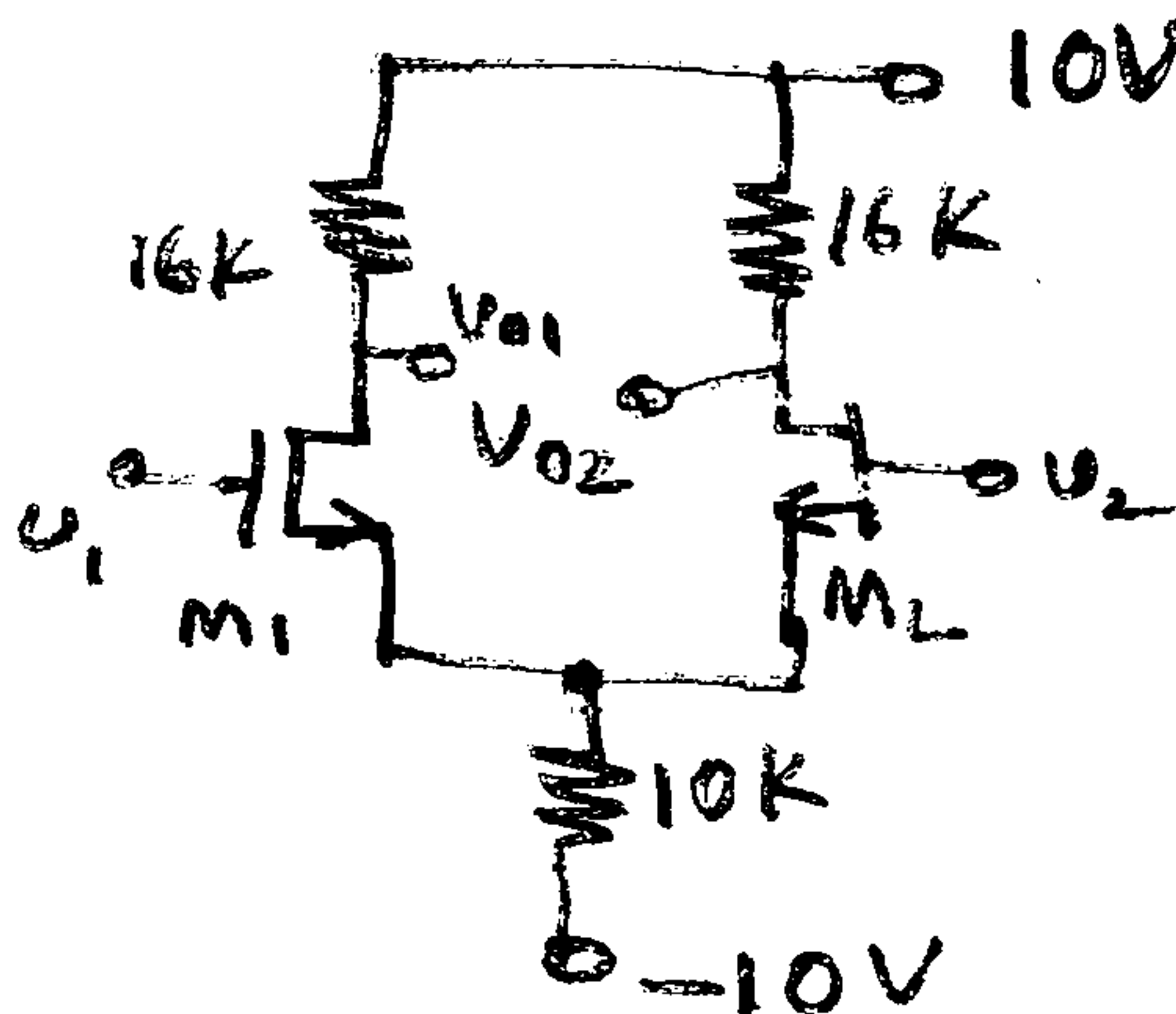- b) The differential amplifier shown in Fig. has $K_{n1} = K_{n2} = 0.1 \text{ mA/V}^2$ and for all transistors, $\lambda = 0$ and $V_t = 1\text{V}$. Draw the equivalent circuit and determine differential gain. 10



Module - III

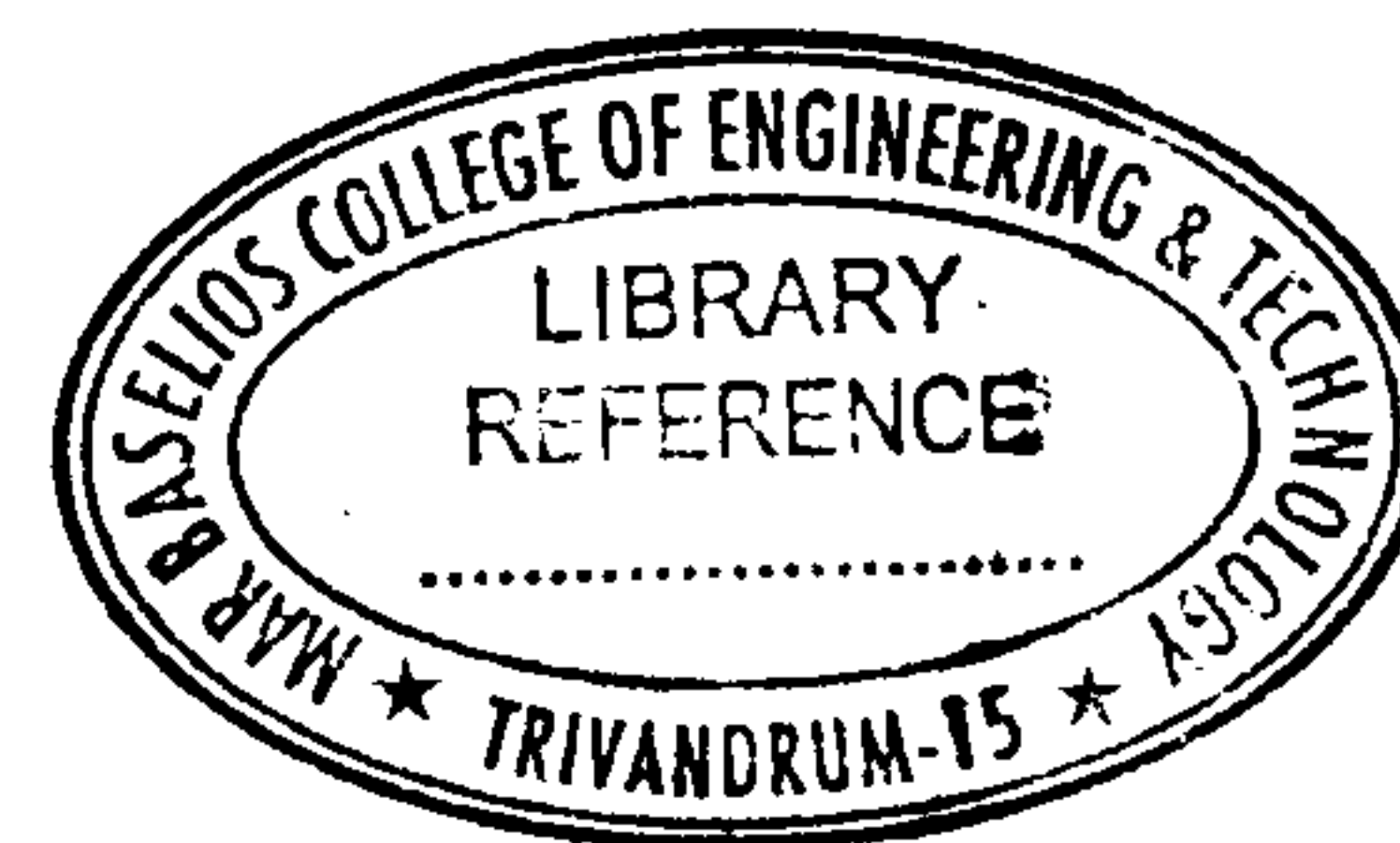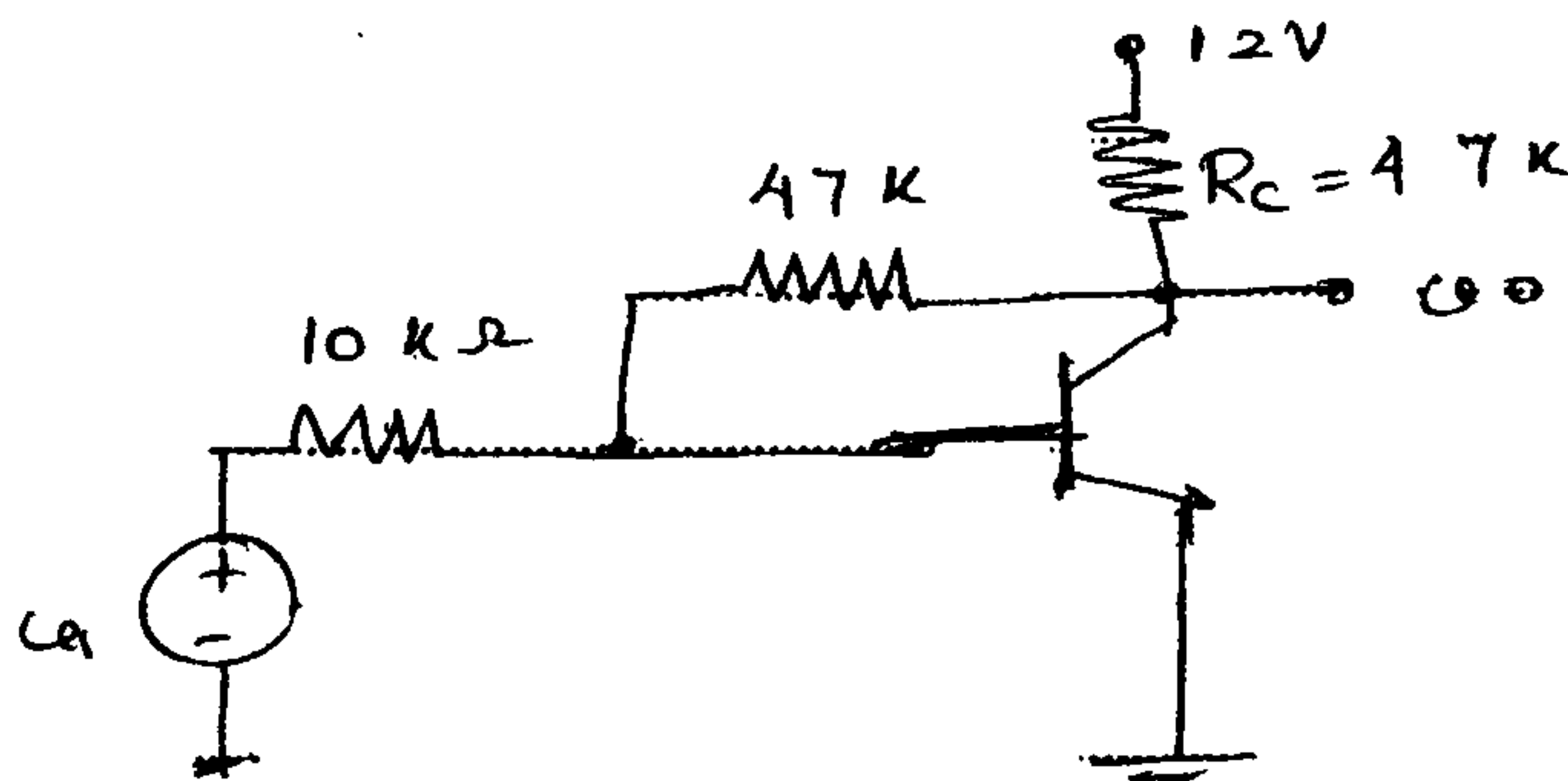15. a) Determine the transconductance gain V_o/I_i of the circuit. Given $\beta = 100$. 10



- b) Explain how crystal oscillator produces stable oscillation. Obtain expression for frequency of oscillation. 10
16. a) Obtain expression for voltage gain of single tuned BJT amplifier. 10
- b) Draw the small signal equivalent of a voltage series feedback amplifier and obtain expression for voltage gain, input resistance and output resistance. 10

Module - IV

17. a) An ideal Class - B push-pull power amplifier with input and output transformers has $V_{CC} = 20\text{V}$, $N_2 = 2N_1$, and $R_L = 20\Omega$. The transistor have $\beta = 20$. For the maximum output signal at $V_m = V_{CC}$, determine : 10
- 1) Output signal power
 - 2) Collector dissipation in each transistor and
 - 3) Conversion efficiency.
- b) Explain with sketches the working of bootstrap circuit. 10
18. a) Draw the circuit of a series voltage regulator and explain its working. 10
- b) Obtain expression for conversion efficiency, total load power, collector dissipation of a transformer coupled Class A power amplifier. 10