

Reg. No. : .....

Name : .....

**Third Semester B.Tech. Degree Examination, October 2016  
(2013 Scheme)  
13.303 : NETWORK ANALYSIS (AT)**


Time : 3 Hours

Max. Marks : 100


**PART – A**

Answer **all** questions. **Each** question carries **2** marks.

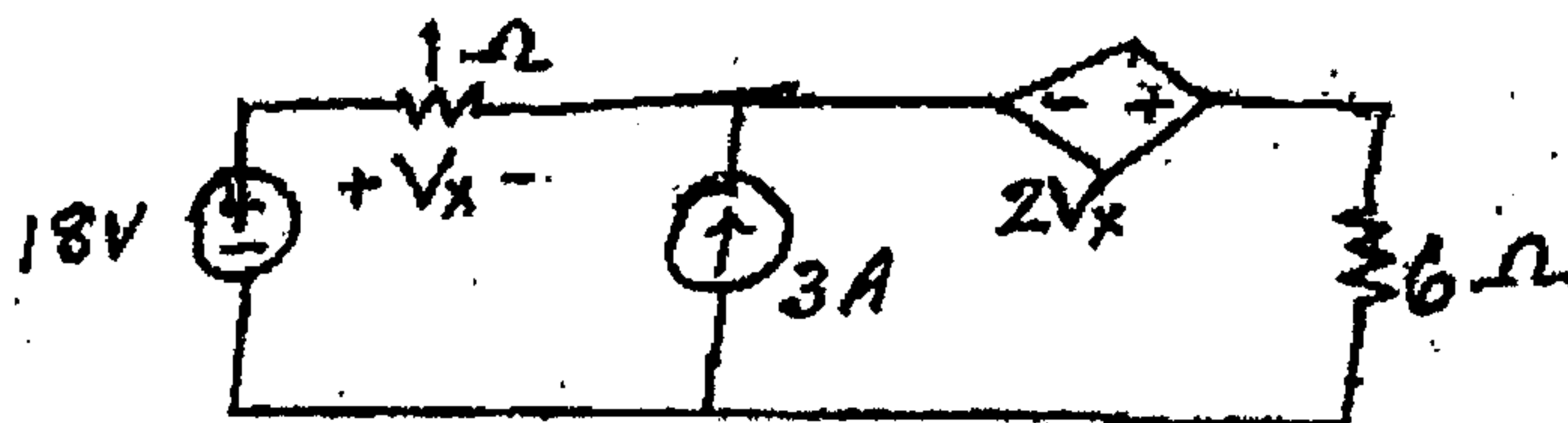1. Explain the fundamental cut-set matrix taking a suitable example.
2. Calculate the current through  $6 \Omega$  resistance in the following circuit.



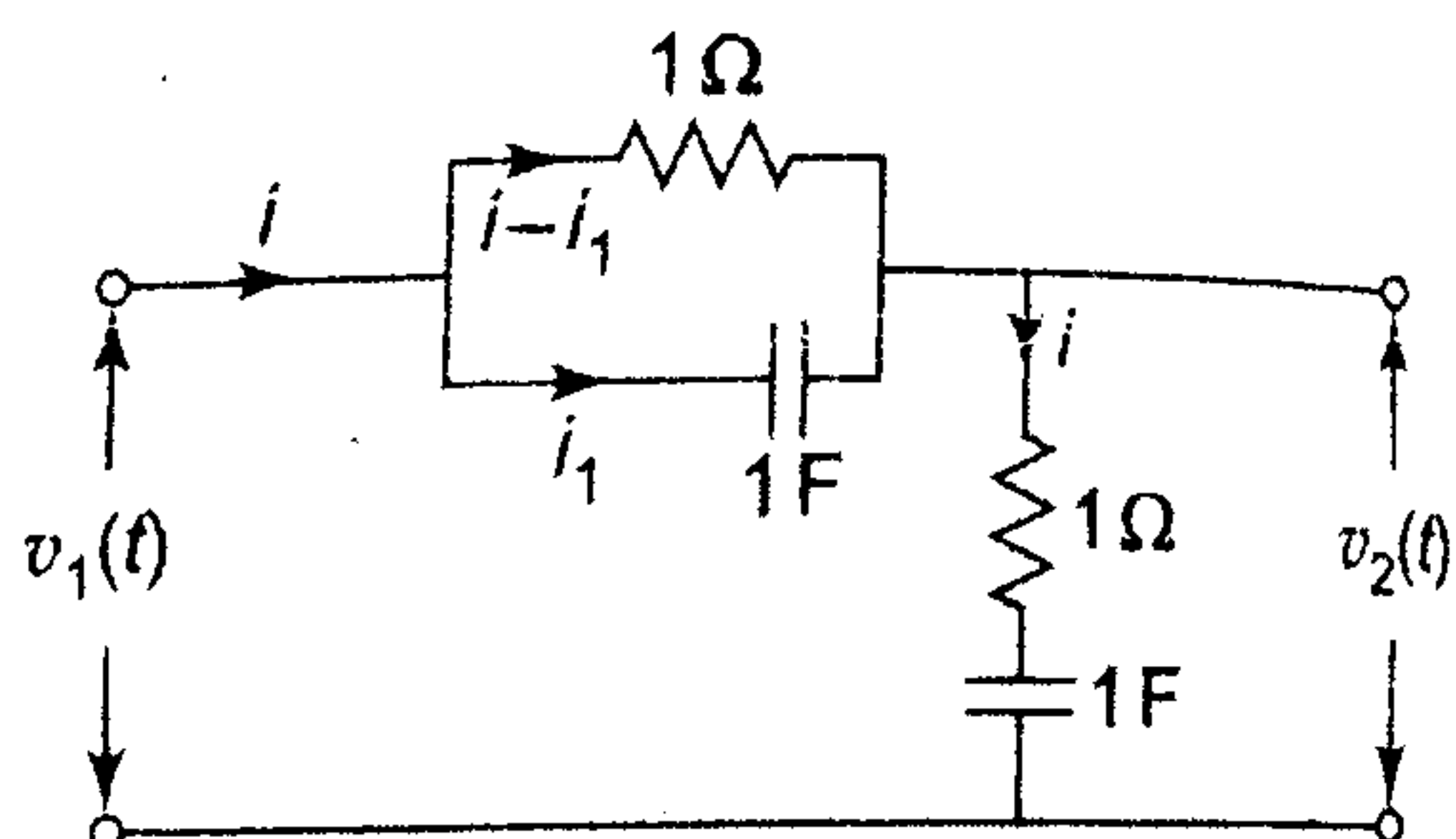3. Plot the following functions :
  - a)  $u(t - 6) + u(t - 4)$
  - b)  $(t - 4) [(t - 1) - u(t - 4)]$ .
4. State the final-value theorem of Laplace Transform and find the final value of the function  $f(t) = 5u(t) + 10e^{-t}$  using final-value theorem.
5. For the following network function, draw the pole zero diagram and hence, obtain the time domain response.  $I(S) = \frac{5s}{(s + 3)(s^2 + 2s + 2)}$ .
6. Obtain the Transfer function of the following network.





7. Define and explain propagation constant and characteristic impedance.
8. A coil is represented by series combination of inductance  $L = 50 \text{ mH}$  and resistance  $R = 15\Omega$ . Calculate the quality factor of the circuit at  $10 \text{ KHz}$ .
9. Check the positive realness of the following functions

a)  $\frac{2s+4}{s+5}$

b)  $\frac{s^2 + 2s + 4}{(s+3)(s+1)}$


10. Analyse the frequency response of reactive one-port network with two external zeros.

PART – B


Answer **any one** question from **each** Module. **Each** question carries **20** marks.

Module – I

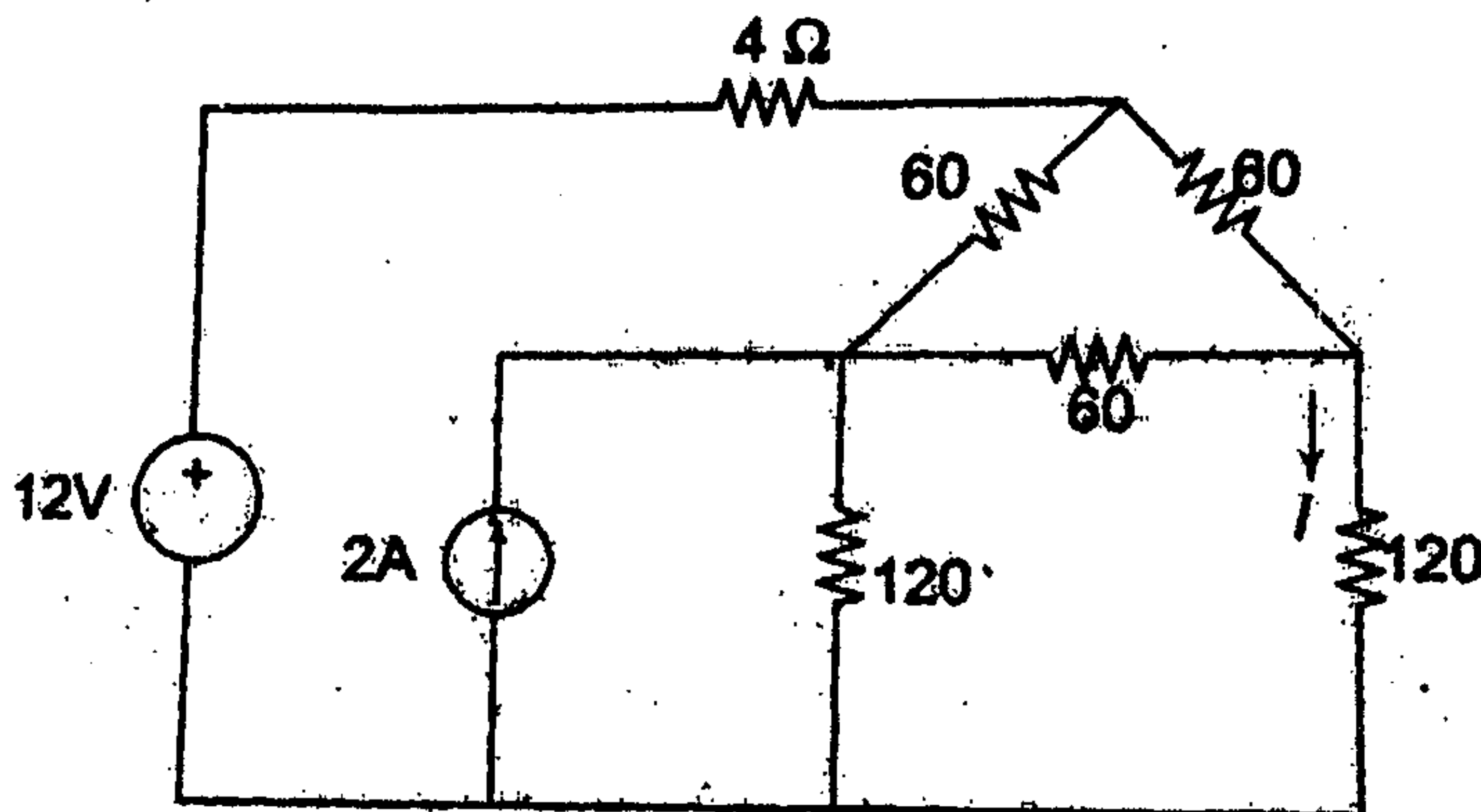11. a) Using nodal analysis, find the current 'I' in the following network.




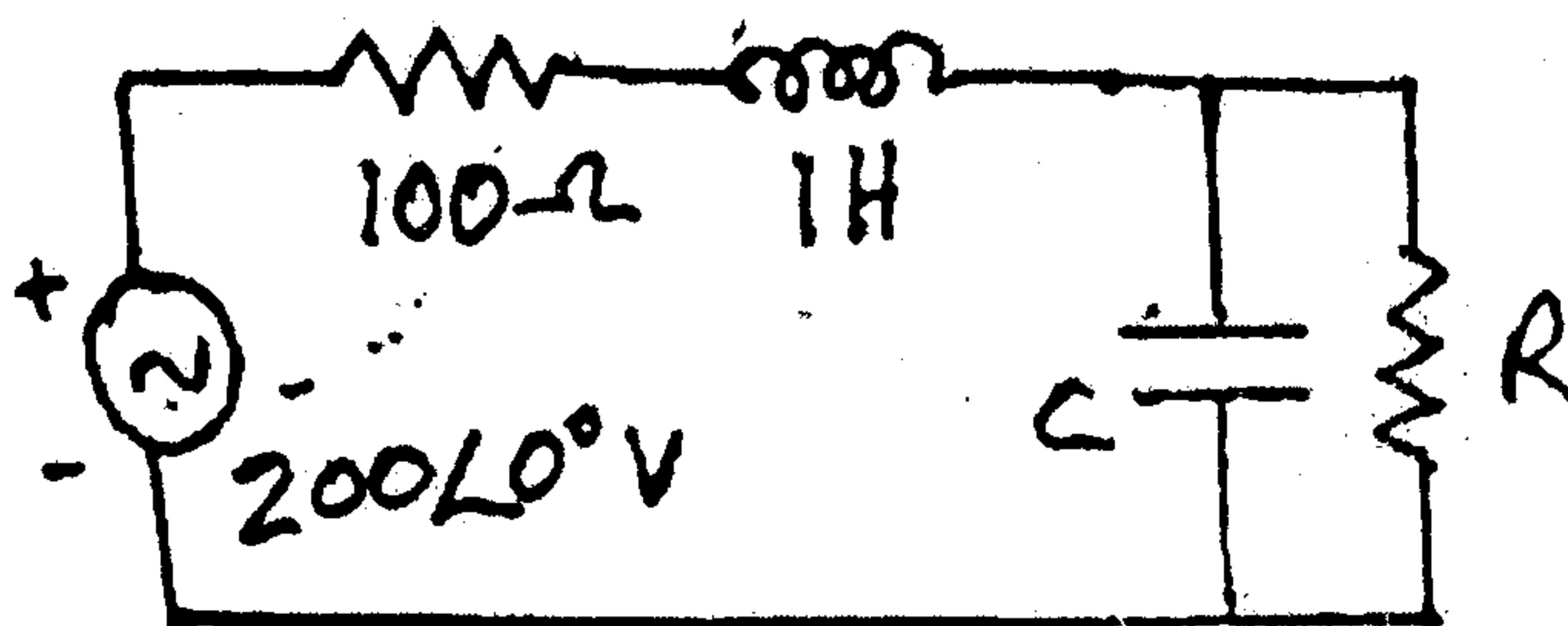- b) Determine the value of  $R$  and  $C$  so that maximum power is absorbed by  $R$  at angular frequency  $200 \text{ rad/sec}$ . in the following network.






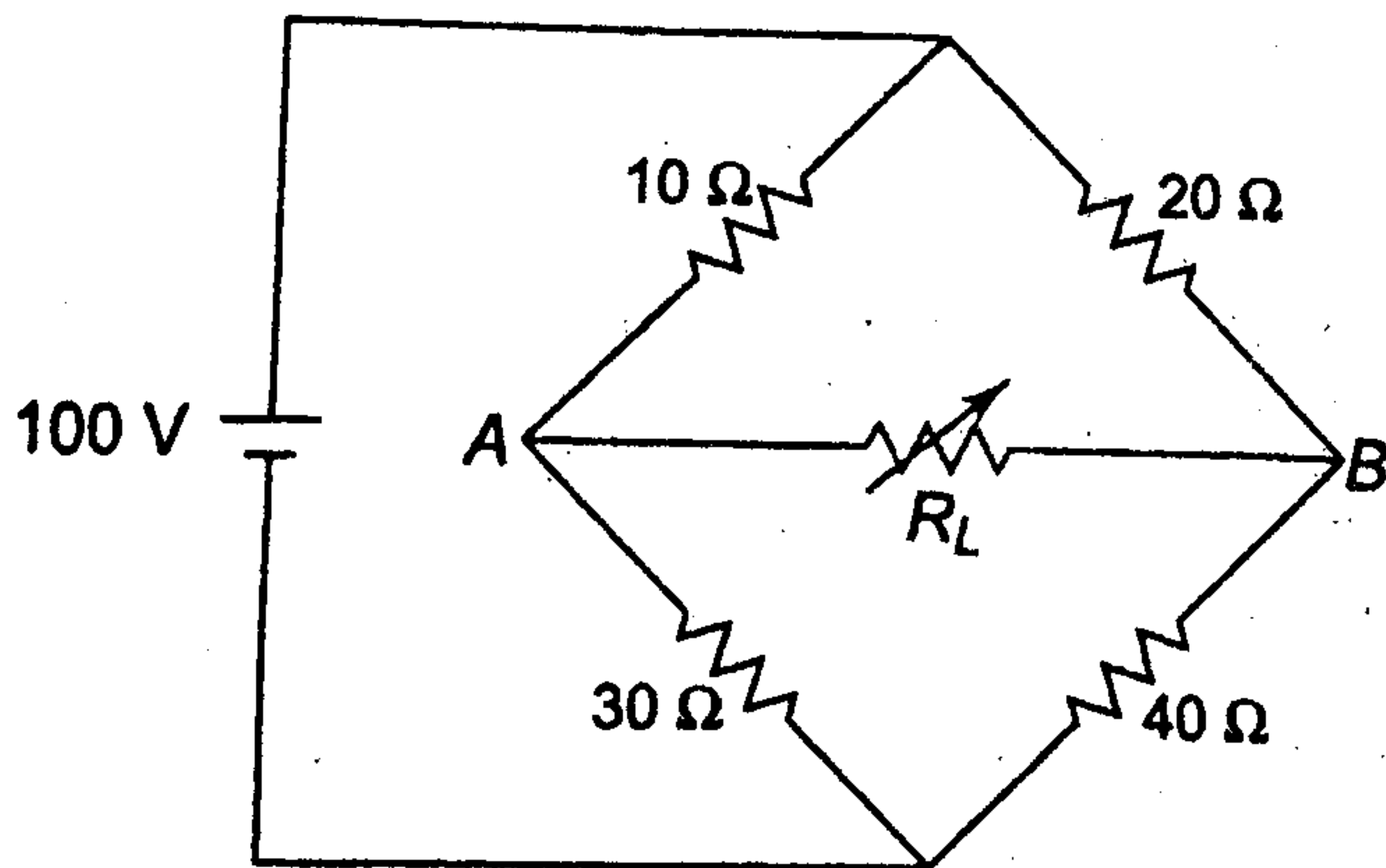12. a) State and prove maximum power transfer theorem.  
b) Determine the load resistance to receive maximum power from the source in the following circuit ; also find out the maximum power delivered to the load.




Module - II

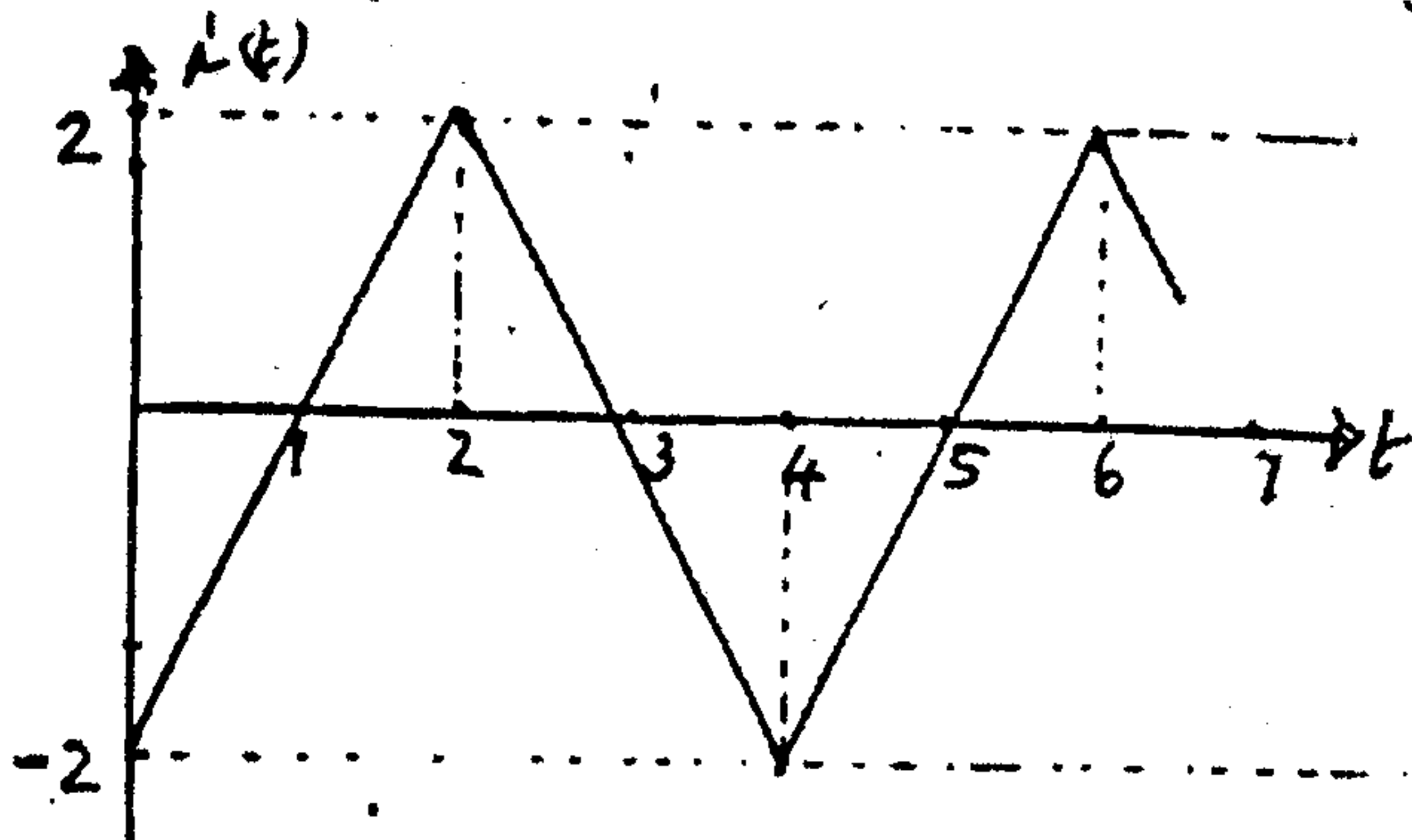13. a) Find the Laplace transform of the following periodic triangular wave.




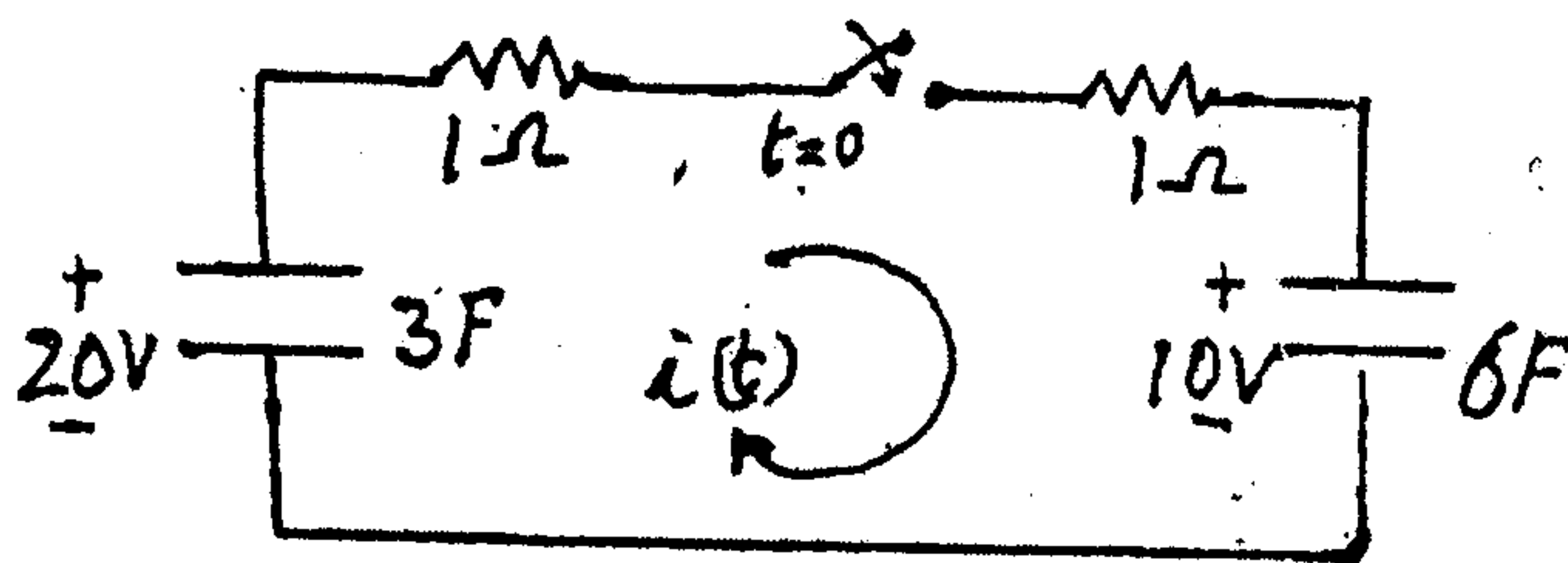- b) In the following network, the switch is closed at  $t = 0$  with capacitance initially energised to the voltages shown in the figure. For the numerical values given, find the expression for the loop current  $i(t)$ .






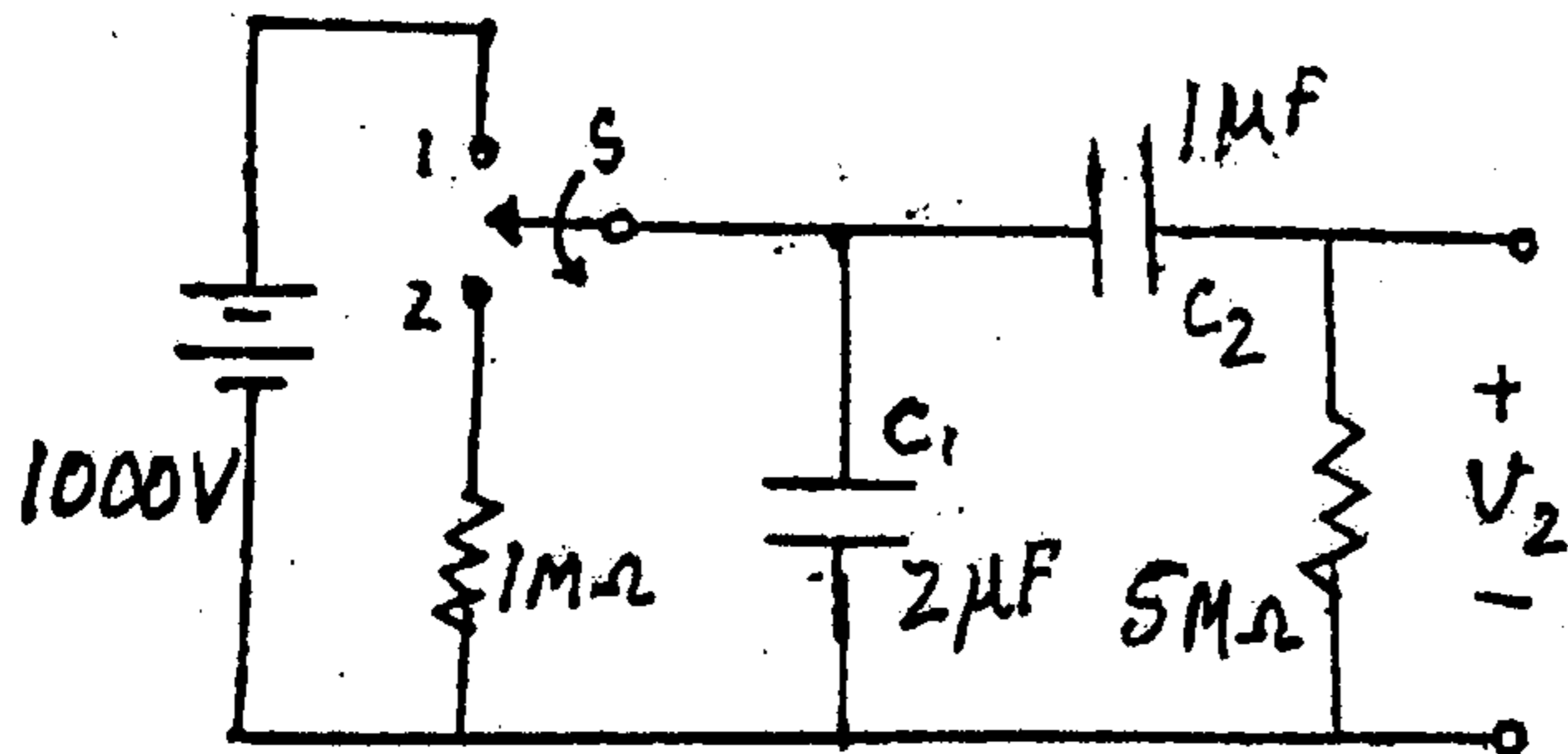14. In the following network, the switch is in position – 1 for long enough to establish steady state condition and at  $t = 0$ , it is switched to position – 2. Find the resulting voltage  $v_2$  across  $5\text{ M}\Omega$  resistor.




**Module – III**

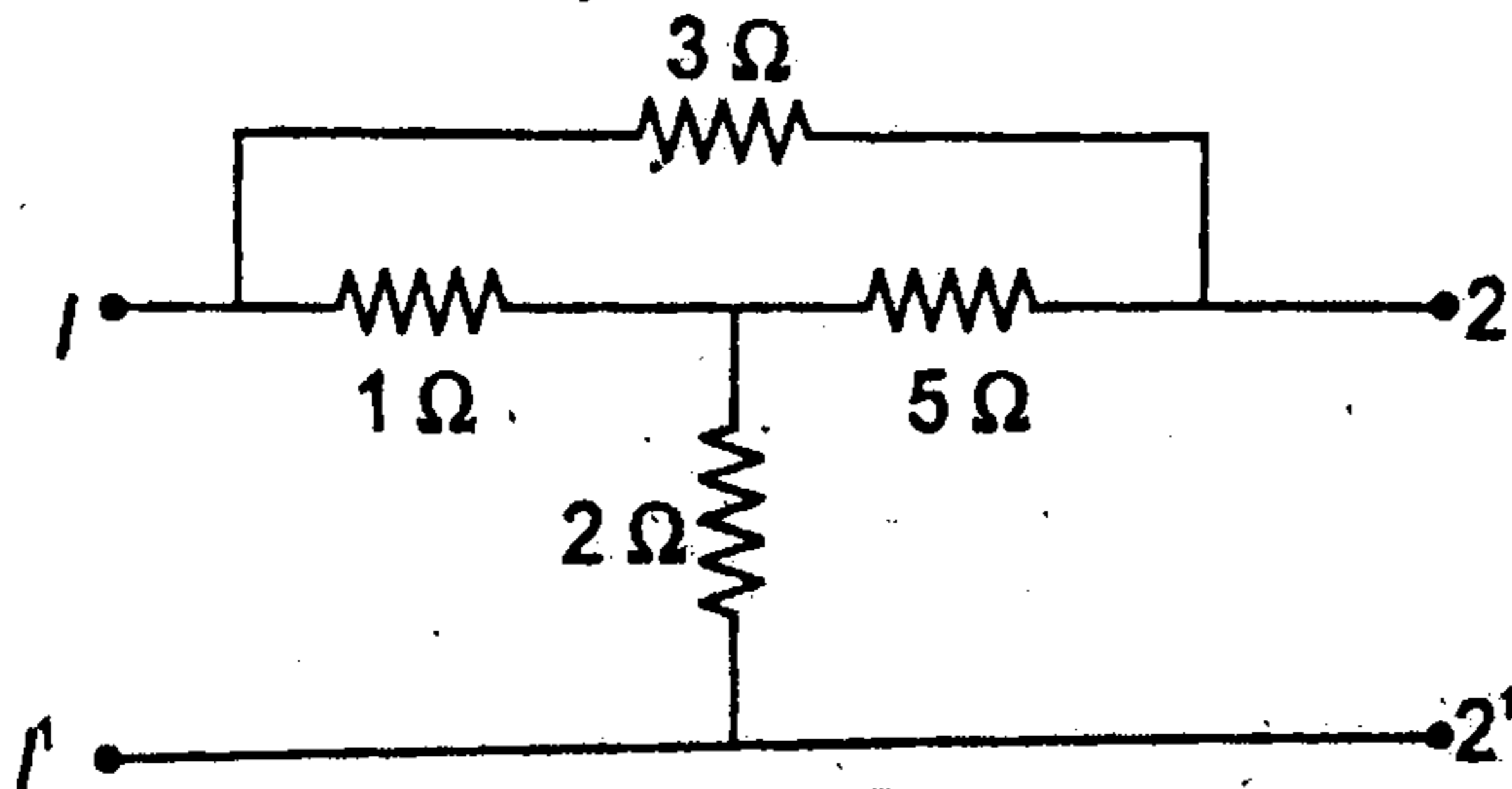
15. Find the ABCD parameters of the following network.



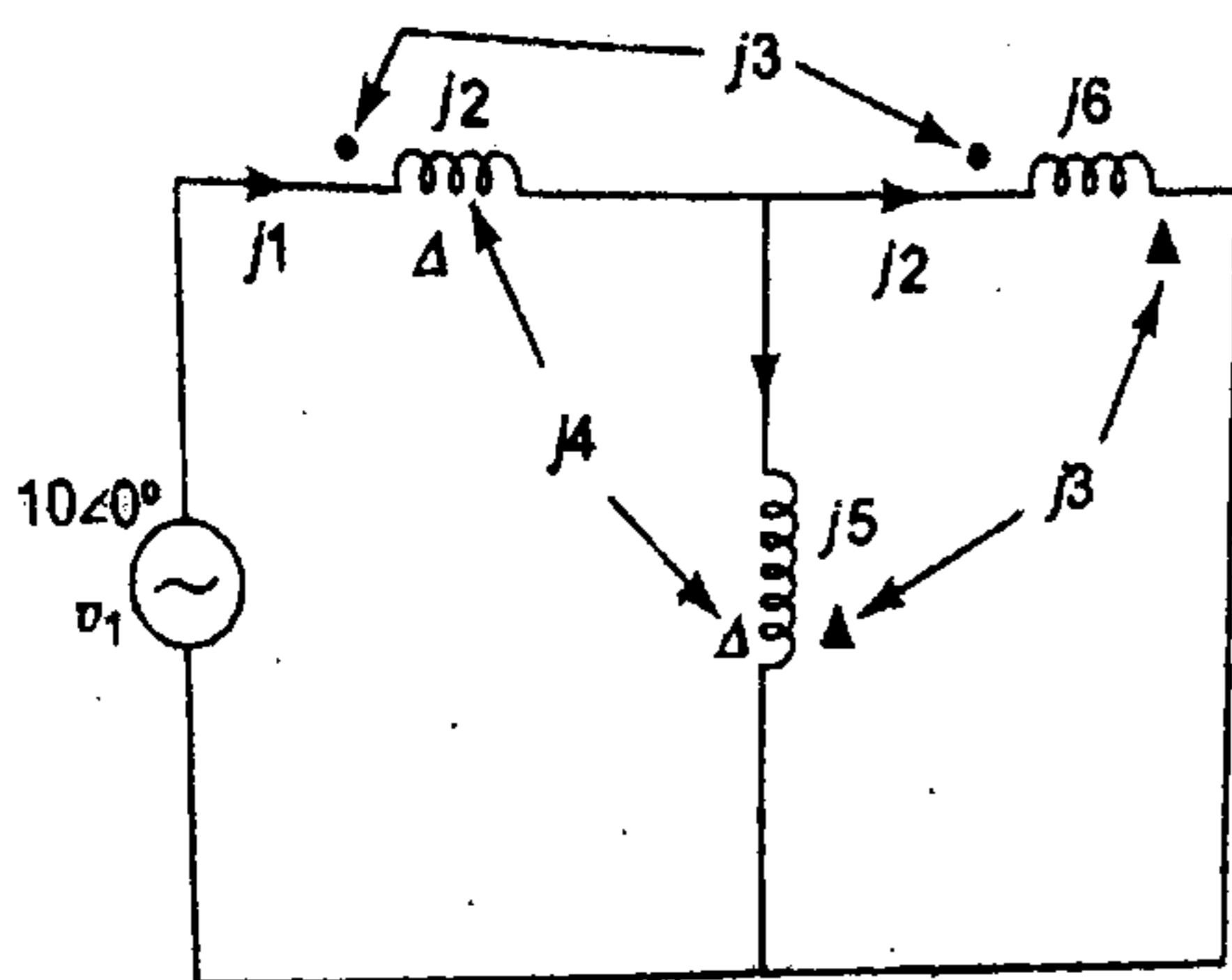16. Write the Mesh equation of the following network.



**Module – IV**

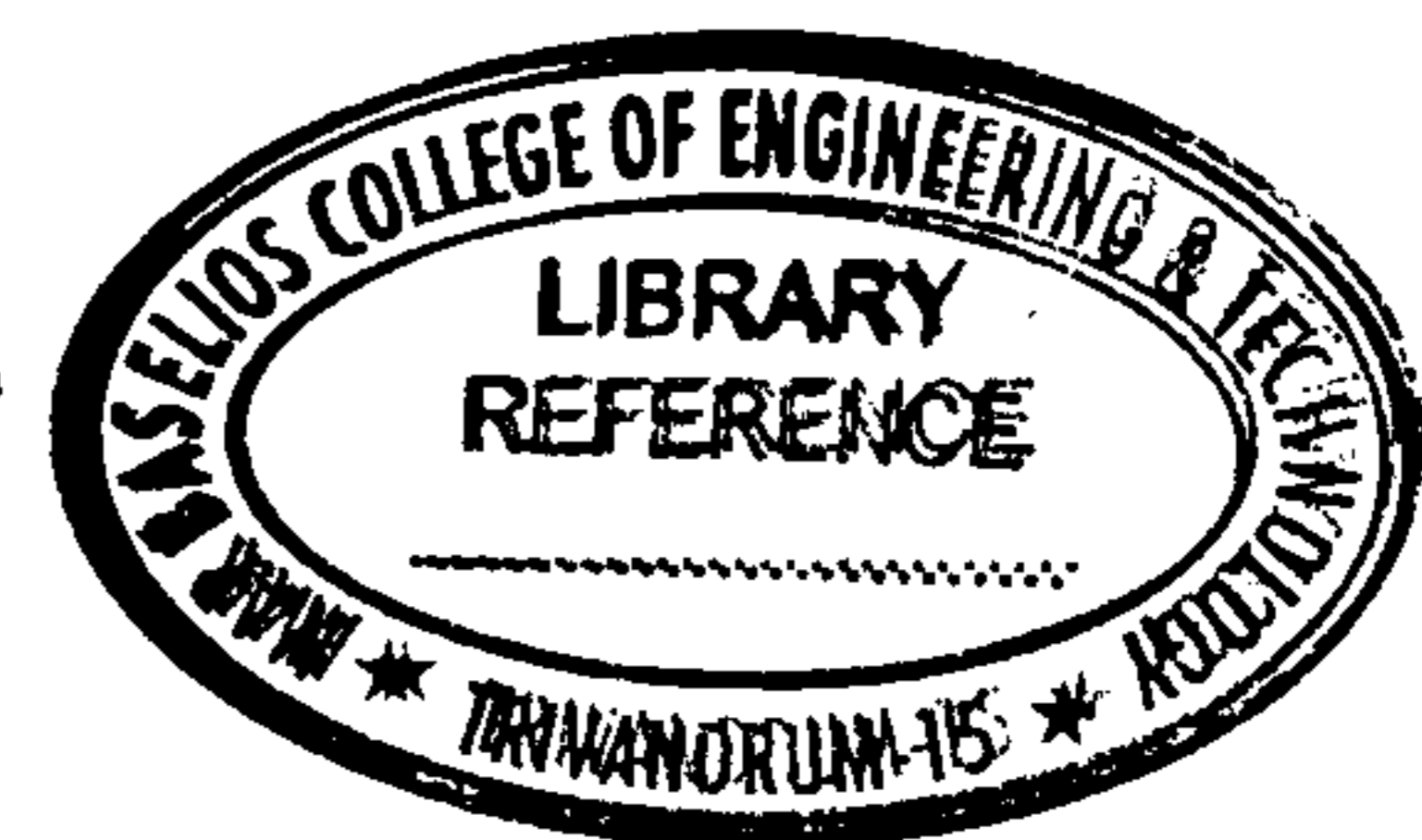

17. A function is given by  $Z(s) = \frac{(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)}$ . Realise it in the first order and second order form of foster LC forms.

18. Find the two Cauer realization of driving-point function given by

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$