



(Pages : 2)



**B – 5233**

Reg. No. : .....

Name : .....

**Combined First and Second Semester B.Tech. Degree  
Examination, February 2017  
(2008 Scheme)**

**08.108 : BASIC ELECTRICAL AND ELECTRONICS ENGINEERING  
(CMNPHTARUFBS)**

Time : 3 Hours

Max. Marks : 100

**PART – A**

Answer **all** questions.

1. State and explain Faradays Laws of Electromagnetic induction.
2. Define RMS value, Average value and form factor in an AC quantity.
3. A circuit consists of  $10\Omega$  resistance  $15\text{ mH}$  inductance and  $281\mu\text{F}$  capacitance in series. The supply voltage is  $110\text{V}$ . Calculate the current when the supply frequency is  $150\text{Hz}$ .
4. Explain Star and Delta connections.
5. What are the different losses in a transformer ? How can they be minimized ?
6. What is the need for High Voltage transmission ?
7. Explain the working of incandescent lamps.
8. Explain the terms dynamic resistance and static resistance of a PN diode.
9. Explain the working of SMPS.
10. Explain the working of protective fuses and ELCB. **(10×4=40 Marks)**

P.T.O.

**PART – B**

Answer **any one** question from **each** Module.

**Module – I**

11. a) State and explain Kirchoff's voltage law and current law. **10**  
b) Explain the terms statically induced emf and dynamically induced emf. **10**
12. With a neat diagram, explain the power measurement in a three phase circuit using two watt meters. Show that the sum of two wattmeter readings gives the total power in the circuit. **20**

**Module – II**

13. a) Explain the working principle of single phase transformer and derive its emf equation. **10**  
b) With the help of circuit diagram explain the working of fluorescent lamp. **10**
14. a) With a neat block diagram, explain the Hydro electric power plant. **10**  
b) Name different methods of wiring for LT installations. Draw the schematic of a typical LT switch board. **10**

**Module – III**

15. a) Explain the working of Zener diode with the help of VI characteristics. **10**  
b) Write short notes on photo diode and LED. **10**
16. a) Draw the circuit diagram and explain the working of a centre tapped full wave rectifier. **10**  
b) Explain the VI characteristics of SCR. **10**
-