



Reg. No. :

Name :

Third Semester B.Tech. Degree Examination, May 2018
(2013 Scheme)
13.303 : NETWORK ANALYSIS (AT)

Time : 3 Hours

Max. Marks : 100

PART – A

Answer **all** questions. **Each** question carries **2** marks :

1. Three equal resistances of 3Ω are connected in star. What is the resistance in one of the arms in an equivalent delta circuit ?
2. State Reciprocity theorem.
3. Give the dual of a circuit containing RLC elements connected in series and excited by voltage V .
4. Sketch the response of RC network for a unit step input.
5. Define time constant of a RL network.
6. State initial and final value theorem of Laplace Transform.
7. A resistance 5Ω , inductance $0.02H$ and capacitor $5\mu F$ are connected in series. Find the resonance frequency.
8. Two capacitances C_1 and C_2 of values $10\mu F$ and $5\mu F$ are connected in series. What is the equivalent capacitance of this combination ?
9. Define propagation constant.
10. Give the expression of h-parameters in terms of Z-parameters.

P.T.O.



PART – B

Answer **any one** question from **each** Module. **Each full** question carries **20** marks :

Module – I

11. a) Determine the current flowing through the load impedance $3 + j4$ using mesh analysis for the network shown in Fig. 11. a). 10

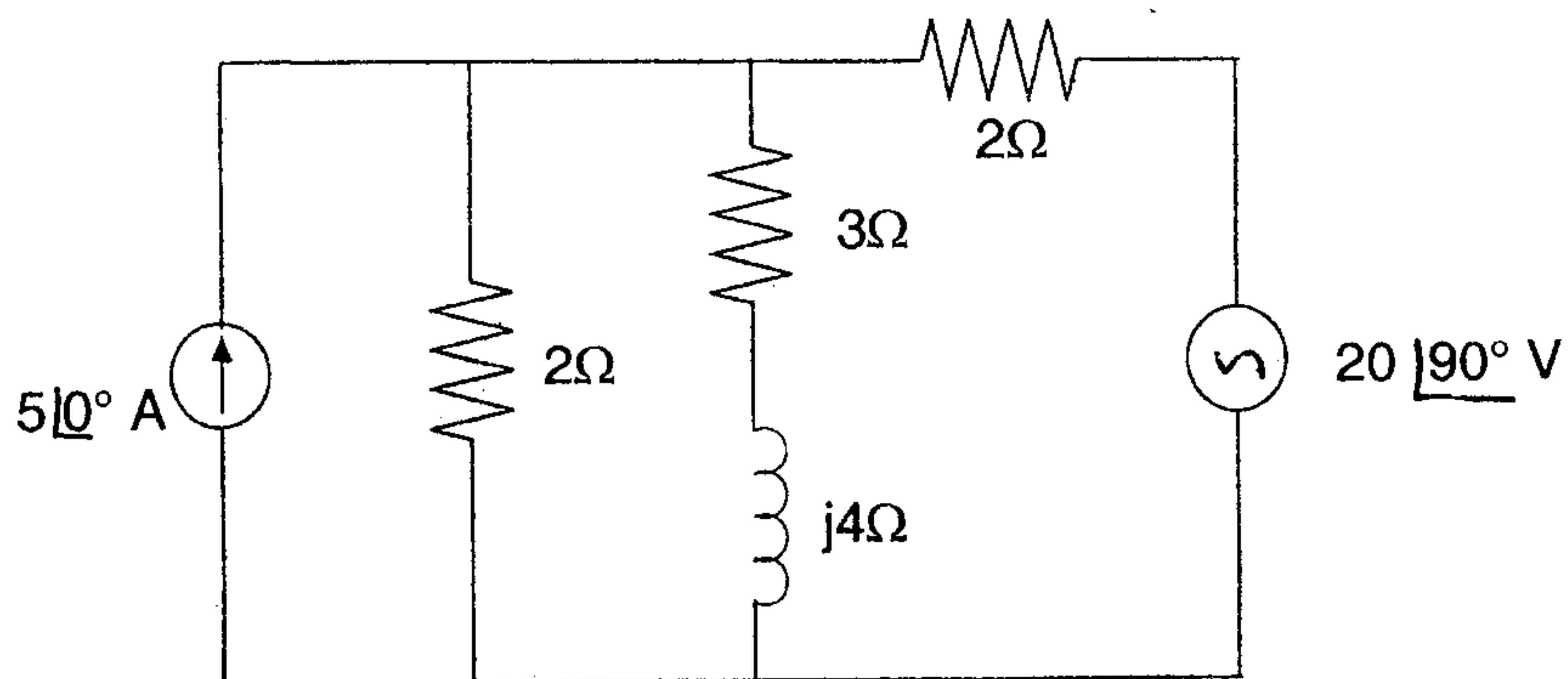


Fig. 11. a)

- b) Explain the following terms as applied to network topology : 10

- i) Oriented graph,
- ii) Tree,
- iii) Link and
- iv) Planar graph and non-planar graph.

12. a) Using superposition theorem, find the current flowing through the load resistance $R_L = 10\Omega$ in the circuit shown in Fig. 12. a). 10

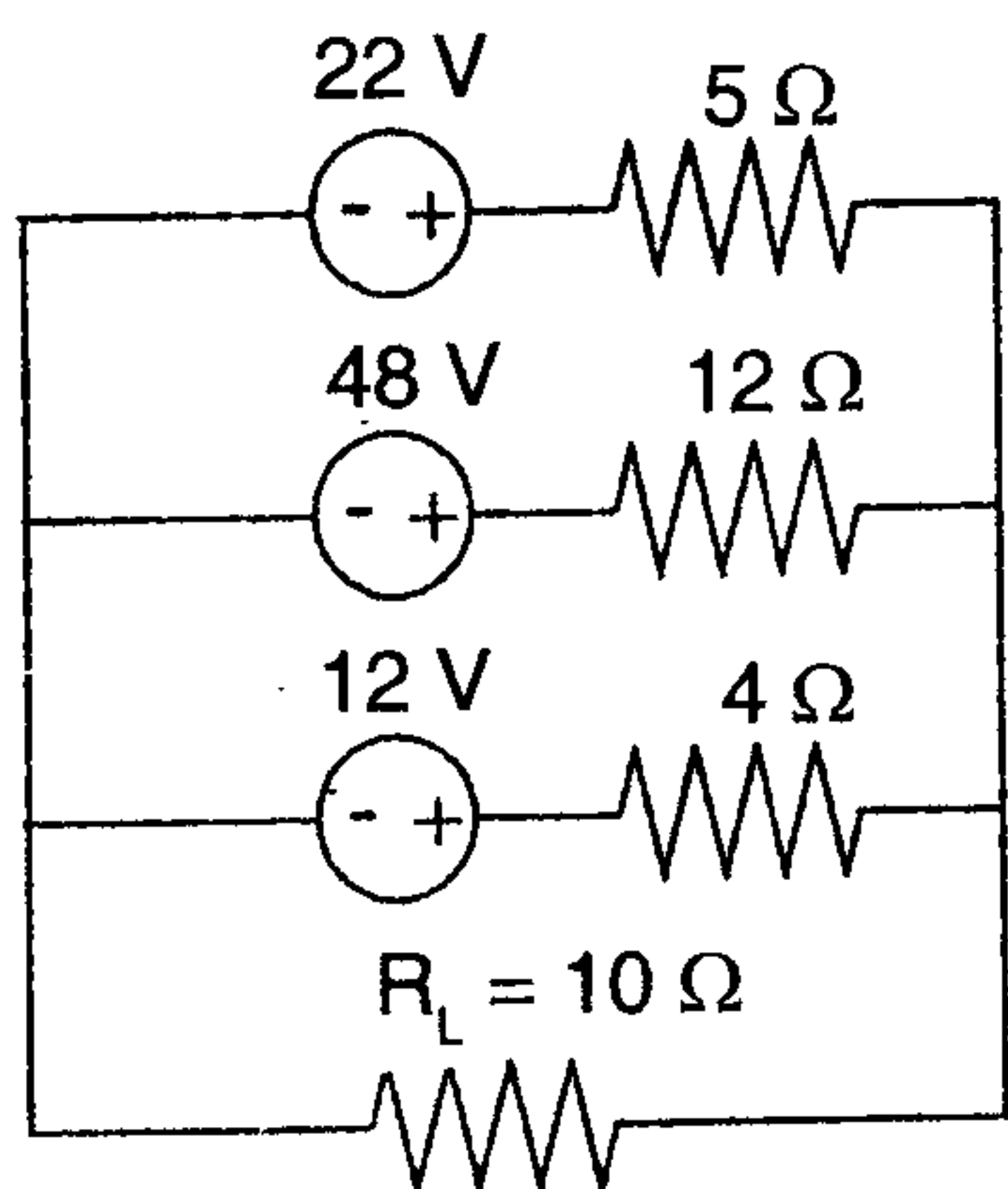


Fig. 12. a)



- b) Obtain the expression for a set of equivalent :
 - i) Star connected impedance to replace a set of delta connected impedances.
 - ii) Delta connected impedance to replace a set of star connected impedances.

10

Module – II

- 13. a) Find the Laplace transform of full wave rectified output as shown in Fig. 13. a).

8

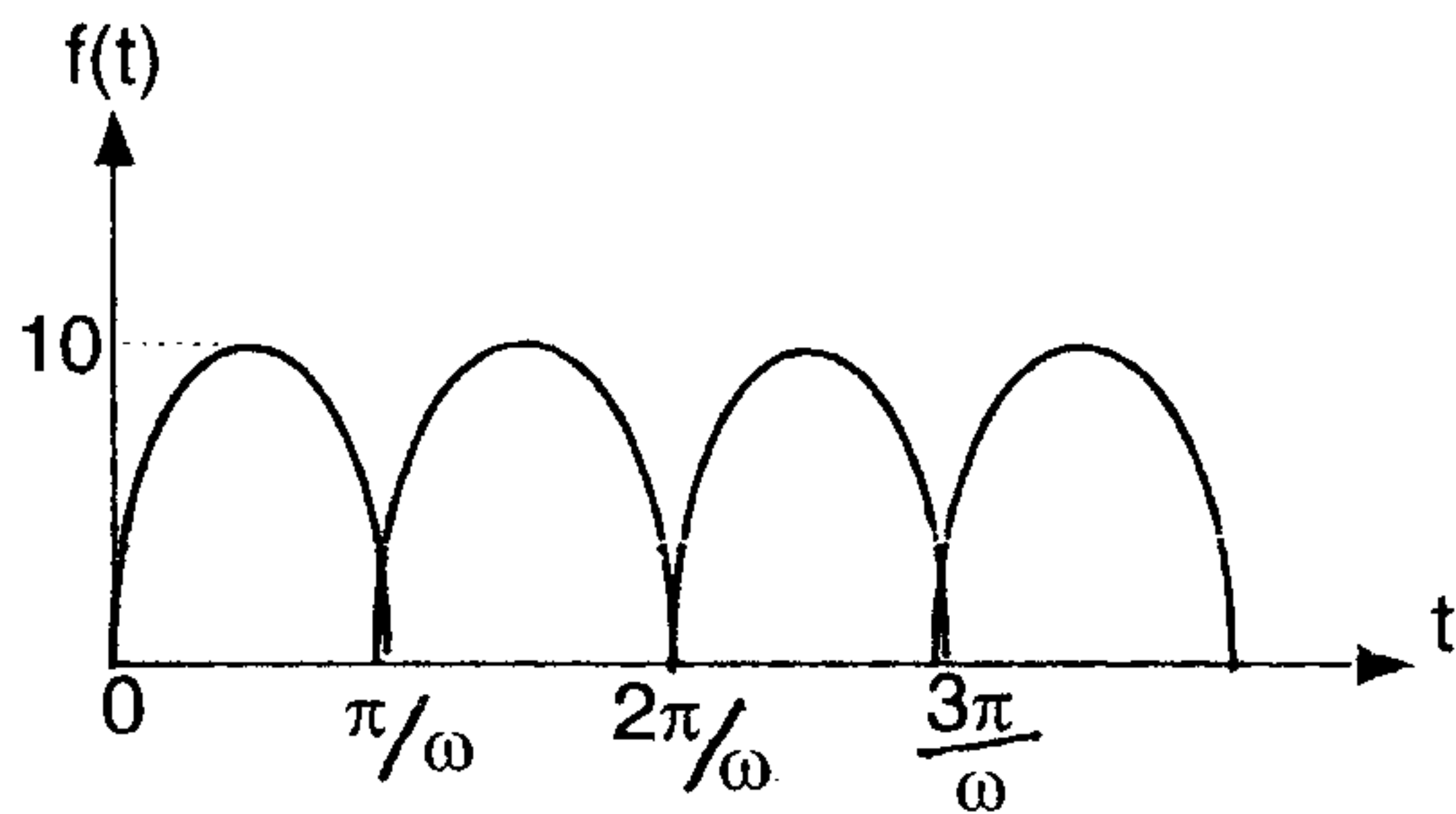


Fig. 13. a)

- b) For the network function $I(s)$, draw the pole zero diagram and hence obtain the time domain response $i(t)$.

$$I(s) = \frac{5s}{(s+1)(s^2+4s+8)}$$

12

- 14. a) For the circuit shown in Fig. 14. a), determine the current delivered by the source when the switch is closed at $t = 0$. Assume there is no initial charge on the capacitor and no initial current through the inductor.

10

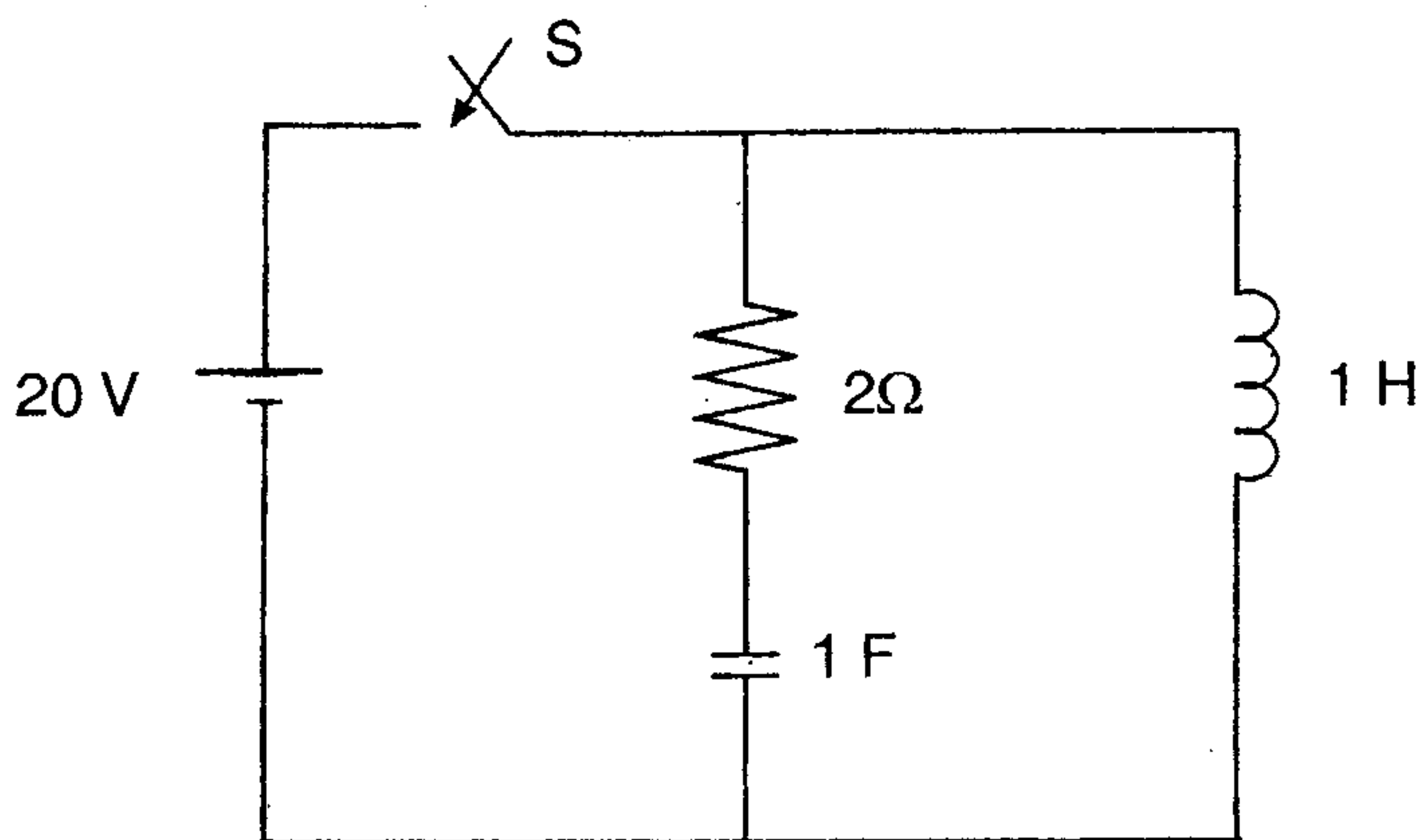


Fig. 14. a)

- b) Derive the Laplace transform of unit step, ramp and impulse functions.

10



Module - III

15. Find the Z and Y parameters for the RC ladder network shown in Fig. 15. 20

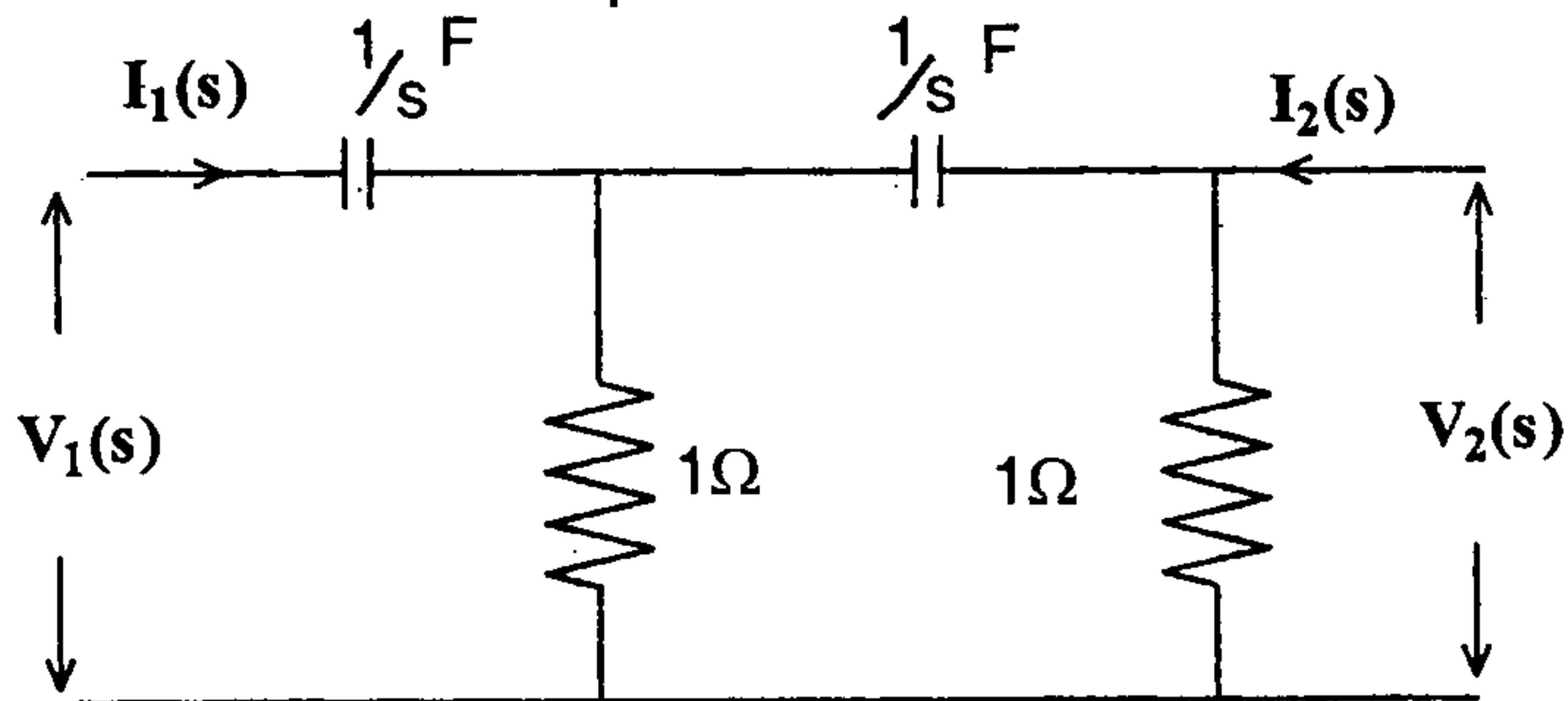


Fig. 15

16. a) Derive the bandwidth for a series RLC circuit as a function of resonant frequency. 12
 b) The resonant frequency of the tuned circuit shown in Fig. 16. b) is 1000 rad/sec. Calculate the self inductances of the two coils and the optimum value of the mutual inductance. 8

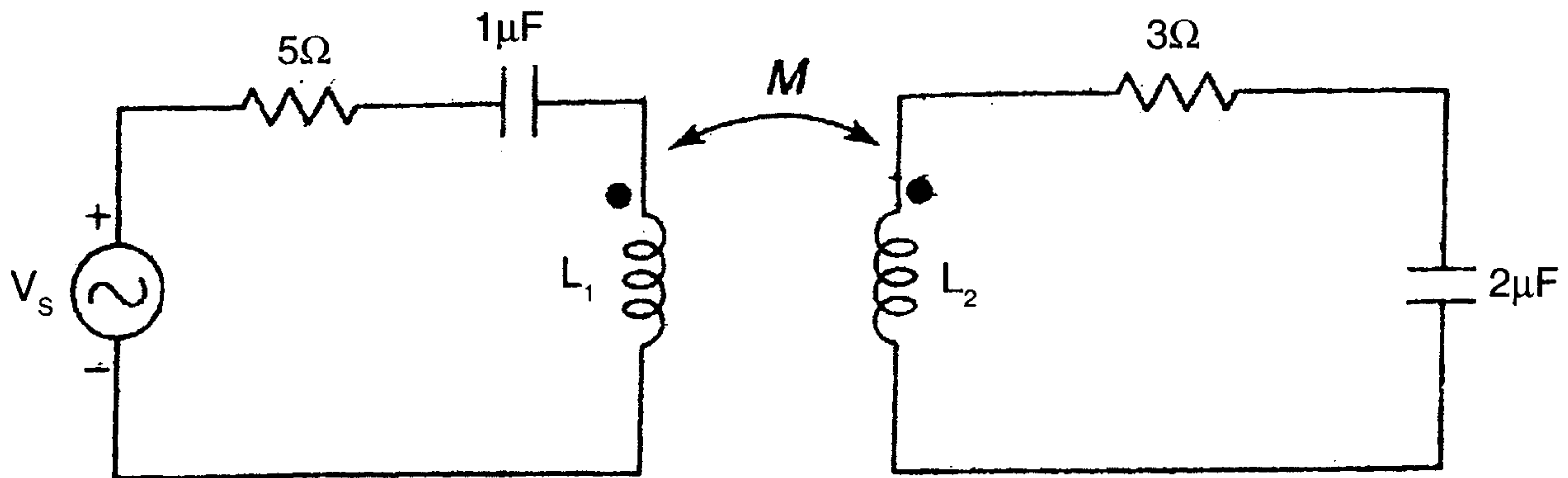


Fig. 16 b)

Module - IV

17. a) Explain the conditions verified for a function $N(s)$ to be a positive real function. 8
 b) Find the two Cauer form realizations of driving point function given by

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s} \quad \text{12}$$

18. a) Find the two Foster form realizations of $Z(s)$

$$Z(s) = \frac{4(s^2 + 1)(s^2 + 16)}{s(s^2 + 4)} \quad \text{12}$$

- b) Check whether $P(s) = S^5 + 3S^3 + 2S$ is a Hurwitz polynomial or not. 8