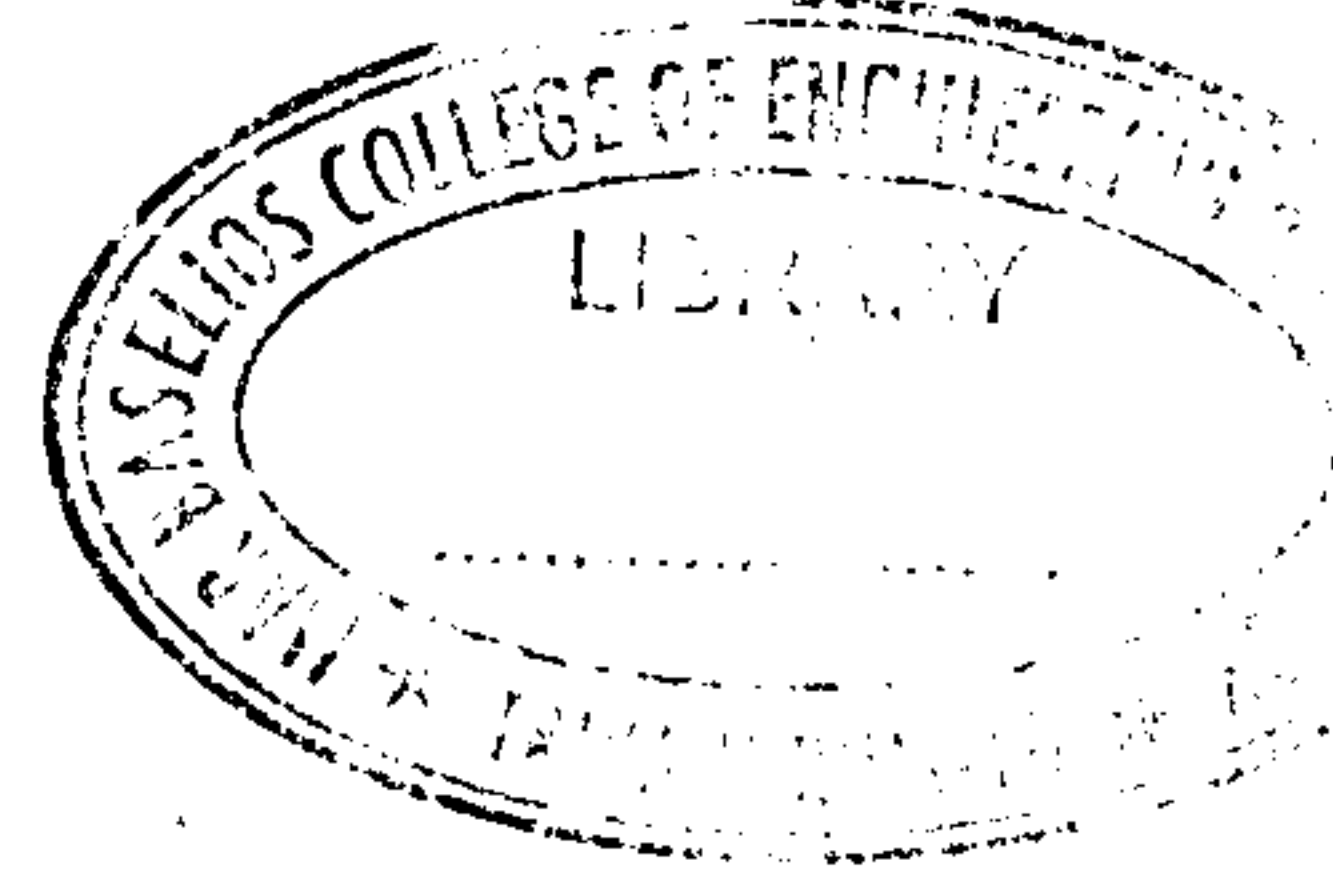




Reg. No. :

Name :

(Pages : 2)



E – 2469

**Eighth Semester B.Tech. Degree Examination, May 2018
(2013 Scheme)**

13.801 : ELECTRICAL DRIVES AND CONTROL (T) ^{EC}

Time : 3 Hours

Max. Marks : 100

PART – A

Answer **all** questions, **each** question carries **2** marks.

1. A DC machine fails to excite. List the various causes for this phenomenon.
2. List the different losses in DC machine. Which of these are constant losses ?
3. Explain why induction motor cannot run at synchronous speed.
4. Compare power MOSFET with IGBT.
5. What is meant by breakdown voltage in BJT ?
6. Define chopper. Give its applications.
7. What is meant by controlled rectifier ? List the applications of controlled rectifier.
8. What is meant by phase-controlled principle ?
9. Mention the purpose of feedback diodes in inverter.
10. List the different methods of voltage control in the inverters. **(10×2=20 Marks)**

PART – B

Answer **one full** question from **each** Module, **each** Module carries **20** marks.

Module – I

11. a) Explain the external and internal characteristics of short-shunt DC compound generator. **10**
- b) A short shunt compound generator delivers a load current of 5A at 230 V and the resistances of armature, series and shunt fields are 0.04 Ω , 0.01 Ω and 500 Ω respectively. Calculate the generated emf and armature current. Allow 1.0 V per brush for contact drop. **10**

OR

P.T.O.



12. a) A 4-pole, 3-phase, 415 V, 50 Hz, 1HP induction motor has frequency in rotor of 2 Hz at full load. At what speed the motor is running and what is its slip. 6
- b) Explain the speed torque characteristics of DC shunt motor, DC series motor; differentially compound long shunt DC motor and cumulative compound long shunt DC motors. 14

Module – II

13. a) Draw and discuss switching characteristics of power MOSFET. 10
- b) Draw and discuss switching characteristics of power BJT. 10

OR

14. a) Explain the principle of operation of step down chopper. Derive the expressions of output voltages. 10
- b) Explain the principle of operation of four-quadrant DC chopper with circuit diagram and draw its VI characteristics. 10

Module – III

15. Describe the operation of a single-phase half-wave controlled bridge rectifier with RL load. Draw the waveforms of output voltage, thyristor voltage and output current. Also derive the output current expression. 20

OR

16. Explain the circulating current mode of working of a single-phase dual converter. List the advantages and drawbacks of circulating mode of operation. 20

Module – IV

17. a) Explain the sinusoidal-pulse width modulation technique of varying the magnitude of output voltage in a single-phase inverter. 10
- b) Explain the multiple-pulse width modulation technique of varying the magnitude of output voltage in a single-phase inverter. 10

OR

18. a) Explain with neat sketch the operation of online and offline UPS. 10
- b) Explain v/f speed control operation of three phase induction motor drive. 10