




(Pages : 3)

F – 5723

Reg. No. :

Name :

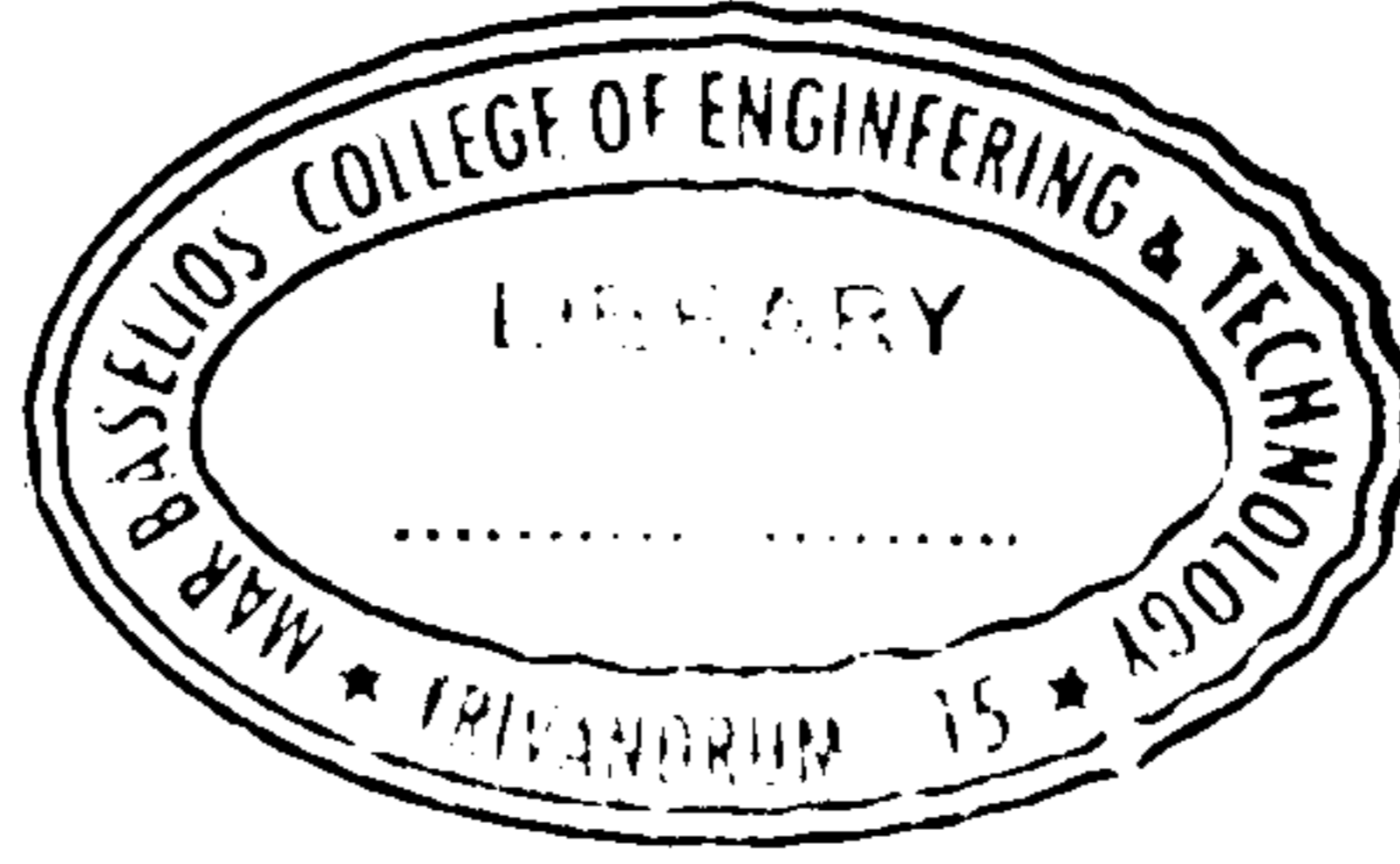

**Third Semester B.Tech. Degree Examination, March 2019
(2013 Scheme)
13.305 : ELECTRONIC CIRCUITS (T)**

Time : 3 Hours

Max. Marks : 100

PART – A

Answer **all** the questions. **Each** question carries 2 marks. **(10×2=20 Marks)**

1. Why is the operating point selected at the centre of the active region ?
2. How are amplifiers classified according to the transistor configuration ?
3. Give the relationship between rise time and bandwidth.
4. Define CMRR.
5. Write the Barkhausen Criteria for Oscillation.
6. Define Transconductance.
7. What is meant by stagger tuning ?
8. What is expression for frequency of oscillation for RC Phase Shift oscillator ?
9. What is Regulator and what are the types of Regulator ?
10. What is meant by Bootstrap circuit ?

P.T.O.



PART – B

Answer **any one full** question from **each** Module. **Each full** question carries **20 marks**. **(4×20=80 Marks)**

Module – I

11. a) Discuss the frequency response characteristics of RC coupled amplifiers. Derive general expression for gain at low, middle and high frequencies. 12
- b) A single stage amplifier has a gain of 60. The collector Load $R_c = 500 \Omega$ and the input impedance is $1 \text{ k}\Omega$, calculate the overall voltage gain when two stages are cascaded through R-C coupling. 8
12. a) Derive the CE short circuit current gain using hybrid $-\pi$ model. 12
- b) A BJT has $h_{ie} = 6 \text{ k}\Omega$ and $h_{fe} = 224$ at $I_c = 1 \text{ mA}$ with $f_T = 80 \text{ MHz}$ and $C_{b'c} = 12 \text{ pF}$. Determine (i) g_m (ii) $R_{b'e}$ (iii) $R_{bb'}$ and (iv) $C_{b'e}$ at room temperature and collector current of 1 mA . 8

Module – II

13. a) Explain in detail the transfer characteristics of differential amplifier. Explain the methods used to improve CMRR. 12
- b) Calculate the drain current and source to drain voltage of a common source circuit. The device parameters are $R_1 = 50 \text{ k}\Omega$, $R_2 = 50 \text{ k}\Omega$, $V_T = -0.8 \text{ V}$ and $K_p = 0.2 \text{ mA/V}^2$. 8
14. a) Draw a common gate MOSFET amplifier and derive expression for voltage gain, current gain, input and output impedance using small signal equivalent circuit. 14
- b) For a common source MOSFET amplifier, the following parameters and circuit components are given. $V_{GS} = 4.66 \text{ V}$, $K_n = 0.4 \text{ mA/V}^2$, $V_T = 3 \text{ V}$, $I_D = 1.11 \text{ mA}$, $R_0 = 40 \text{ k}\Omega$. 6

Module – III

15. a) Draw the small signal equivalent circuit of a series feedback amplifier and derive the expression for input resistance, output resistance and voltage gain with feedback. 12
- b) A Colpitt's oscillator is designed with $C_1 = 100 \text{ pF}$ and $C_2 = 7500 \text{ pF}$. The inductance is variable. Determine the range of inductance values, if the frequency of oscillations is to vary between 950 kHz and 2050 kHz . 8
16. Draw the circuit of a Wein bridge oscillator and explain its working. Derive the expression for frequency of oscillation and condition for oscillation. 20



Module – IV

- 17. a) Draw the circuit of Class A power Amplifier and explain its operation. Derive the expression for efficiency of Class A power Amplifier. **12**
- b) Determine the Overall efficiency of Class B power Amplifier when $V_{CC} = 20V$ and $V_{ce\min} = 2.5V$. **4**
- c) Explain harmonic Distortion in Power Amplifier. **4**
- 18. a) With relevant sketches explain the working of Current sweep circuits. **10**
- b) A half wave rectifier has a load resistance of $3.5\text{ k}\Omega$. If the diode and secondary of the transformer have a total resistance of $800\ \Omega$ and the input voltage has an ac signal of 240 V (peak value). Determine (i) Peak, average and RMS values of current flowing (ii) DC power output (iii) AC power input (iv) Rectification efficiency and (v) Ripple factor. **10**

